

Full Name: Orkun K  k

Course Code: EEE202

Section: 02

Experiment Number: 01

Date: 15.10.2023

## Lab 1: Time-Domain and Frequency-Domain Analyses in LTSpice

### Software Implementation

#### Introduction (Part 1):

For Part 1, main purpose of the experiment is analyzing the behavior of the output voltage regarding a input voltage. It consists of 2 parts, where in the first part, a voltage divider circuit is designed and the behavior of the output voltage is viewed. In the second part, an inductor is swapped with one of the resistors and output voltage is analyzed regarding different frequency values given from the input voltage.

#### Methodology (Part 1.1):

In the first part (Part 1.1), It is asked to create a simple voltage divider circuit in LTSpice and analyze its behavior.

I choose the following voltage and resistor values for this experiment:

$$R_1 = 6 \, \Omega$$

$$R_2 = 12 \, \Omega$$

$$V = 6V \text{ sinusoidal with } 10 \text{ kHz}$$

 


Figure 1.1: Schematic of the first circuit

#### Analysis:

From the voltage divider formula:

$$V = V_1 \times \frac{R_2}{R_1 + R_2}$$

Eq. 1: Voltage Divider Formula

I calculated the voltage on  $R_2$  to be 4V.

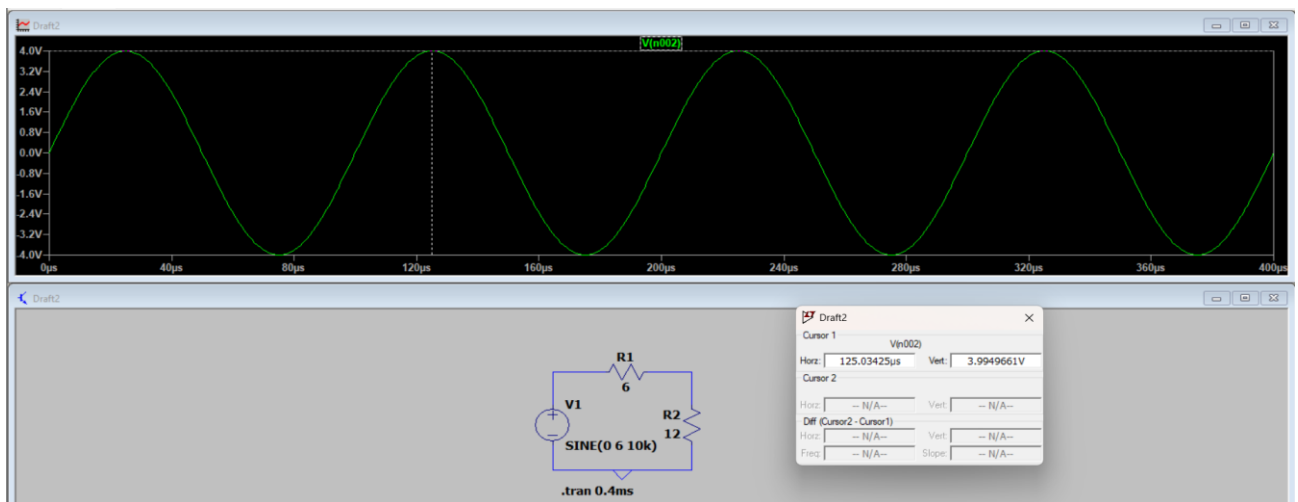


Figure 1.2: Output Voltage at  $R_2$

In the simulation, the result came out to be 3.994 Volts which is very close to 4 Volts.

Calculation	Simulation
$V_{Out} = 4 \text{ V}$	$V_{Out} = 3.994 \text{ V}$

Table 1: Comparison of calculation and simulation datas for Part 1.1

### Methodology (Part 1.2):

In the second step of first part (Part 1.2), it is asked to design a RL circuit by replacing the  $R_2$  in Figure 1.1 with an inductor.

In this step, I choose the following values:

$$R_1 = 20 \Omega$$

$$L_1 = 10 \mu\text{H}$$

 


Figure 1.3: RL Circuit that is designed

### Simulation:

For 8 V input with 100 kHz, the plot (Figure 1.4) shows that while the input voltage is 8 Volts, the output voltage is only about 2.4 Volts.

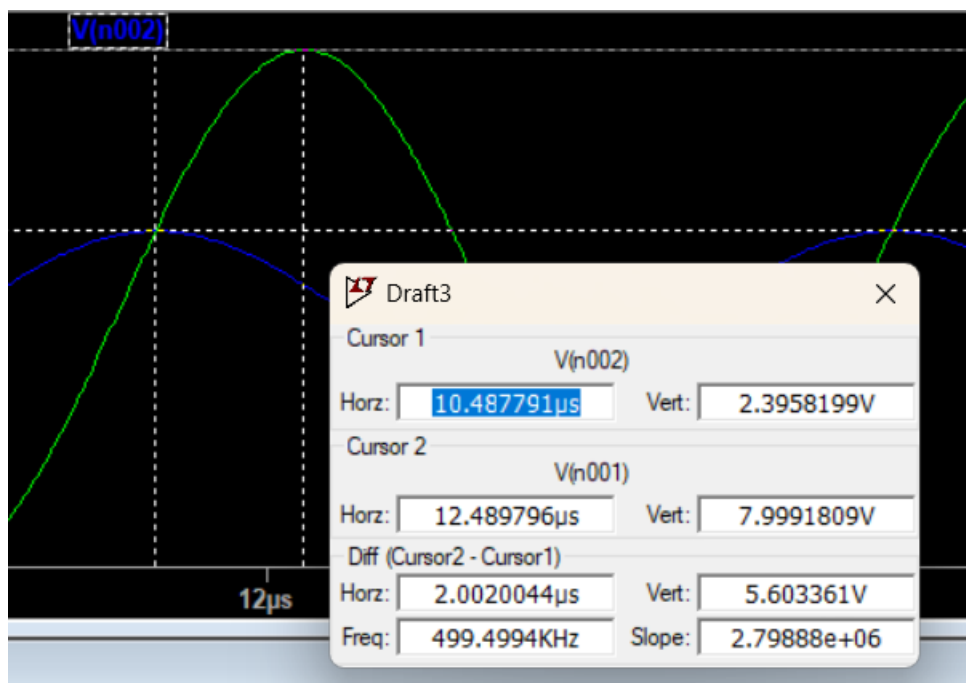


Figure 1.4: Input and Output Voltages for 8 V 100kHz voltage source

For 8 V input with 500 kHz, the plot (Figure 1.5) shows that while the input voltage is 8 Volts, the output voltage is 6.7 Volts.

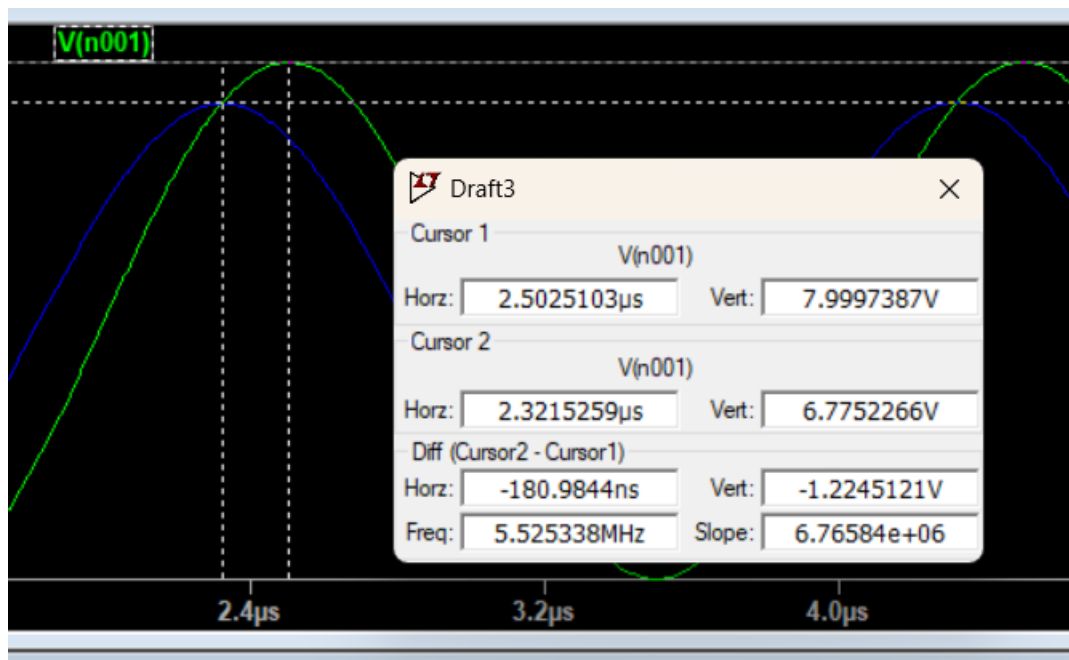


Figure 1.5: Input and Output Voltages for 8 V 500kHz voltage source

For 8 V input with 10 kHz, the plot (Figure 1.6) shows that while the input voltage is 8 Volts, the output voltage is only about 251 mV.

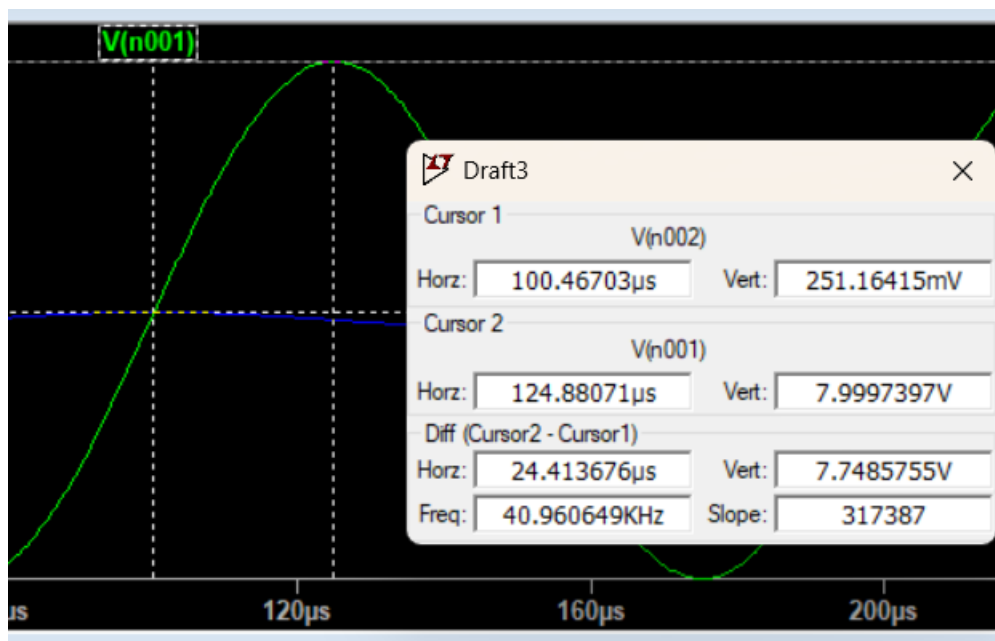


Figure 1.6: Input and Output Voltages for 8 V 10kHz voltage source

$V_{in} = 8 \text{ Volts } 500 \text{ kHz}$	$V_{out} = 6.7 \text{ Volts}$
$V_{in} = 8 \text{ Volts } 100 \text{ kHz}$	$V_{out} = 2.4 \text{ Volts}$
$V_{in} = 8 \text{ Volts } 10 \text{ kHz}$	$V_{out} = 251 \text{ mV}$

Table 2: Input and Output voltages regarding different frequency values for Part1.2

As seen from the results, when the frequency increases, the output voltage also increases, and when the frequency decreases, output voltage also decreases. Therefore, this circuit acts like a high-pass filter.

### Methodology (Part 2):

In this part of the experiment, AC (frequency domain) analysis is asked. Main purpose of this part is examining the change in the output voltage regarding the frequency change in a Logarithmic plot because we want to observe the circuits behavior in a long frequency interval, therefore AC small signal analysis is used.

 


Figure 2.1: RL circuit with small signal AC analysis

### Simulation:

The plot of the output voltage at  $L_1$  in decibels can be seen in Figure 2.2.

 


Figure 2.2: Logarithmic plot of output voltage at  $L_1$  of the circuit in Figure 2.1

Using the cursor at the LTSpice, -3dB point (cutoff frequency) is found to be 319 kHz. (Figure 2.2)

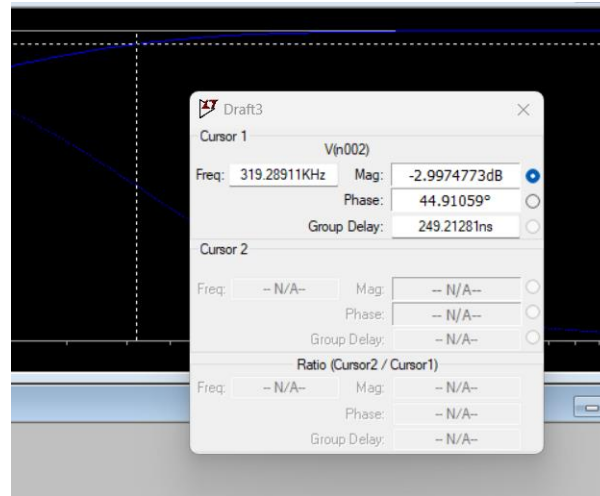


Figure 2.3: -3dB cutoff frequency of circuit in Figure 2.1

Because signal generators in the lab have a serial output resistance of 50  $\Omega$ , I added a 50  $\Omega$  serial resistance to  $R_1$ .

 


Figure 2.4: circuit in Figure 2.1 with an extra 50  $\Omega$  resistance

The output voltage at  $L_1$  is plotted on dB scale in Figure 2.5.

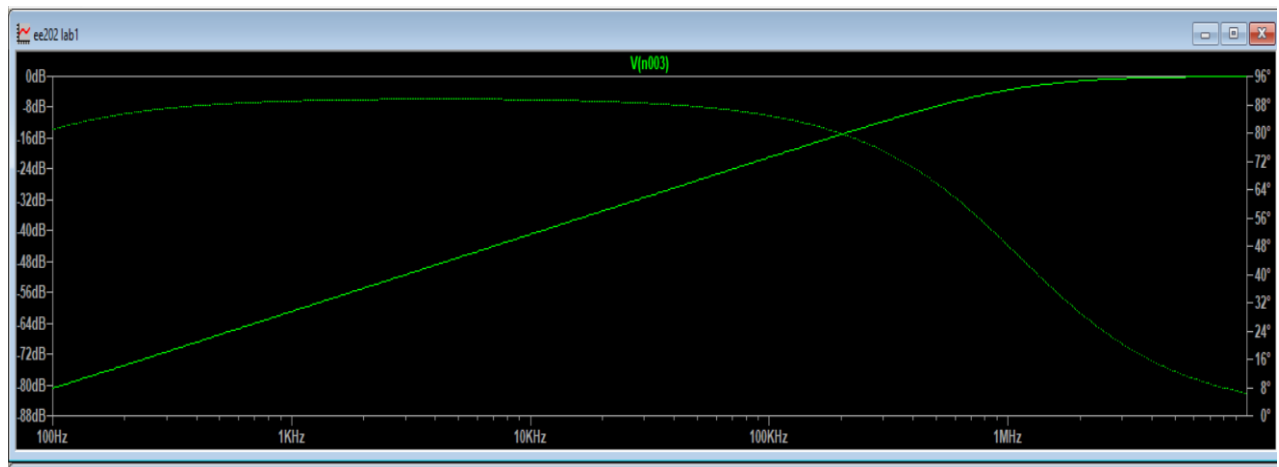


Figure 2.5: Logarithmic plot of output voltage at  $L_1$  of the circuit in Figure 2.4

Again using the cursor at LTSpice, -3dB point (cutoff frequency) is found to be 1.11 MHz. (Figure 2.6)

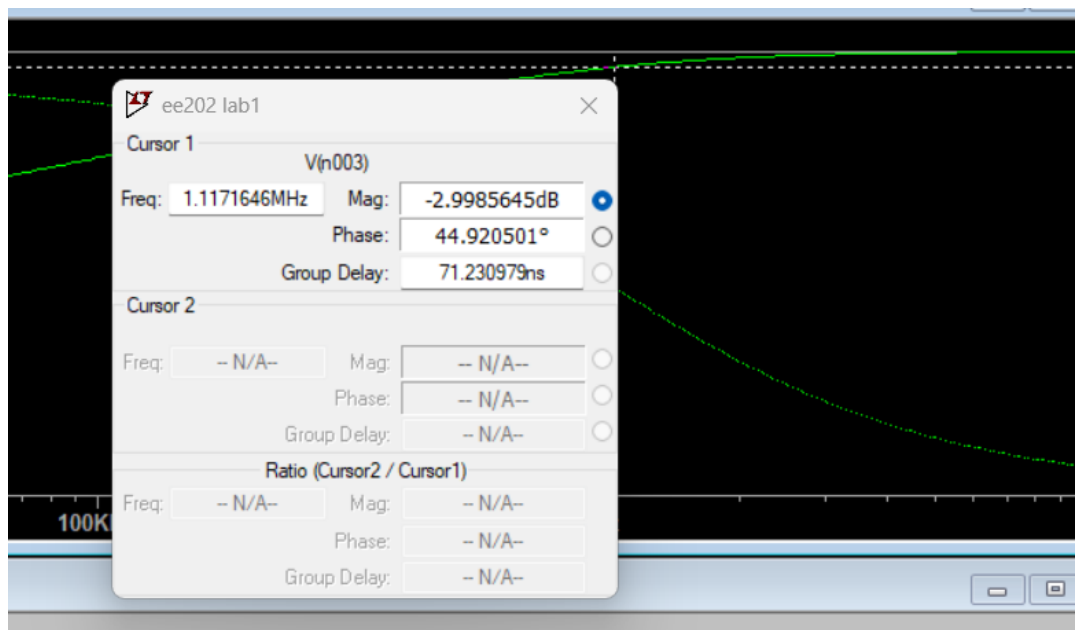


Figure 2.6: -3dB cutoff frequency at the output voltage at  $L_1$  of the circuit in Figure 2.4

Next, I choose the input voltage to be the voltage between 50  $\Omega$  and 20  $\Omega$ , and plotted the ratio of the output voltage and input voltage. (Figure 2.7)

 


Figure 2.7: ratio of the output at  $L_1$  and input voltage at  $R_1$  and  $R_2$ .

Circuit type	$V_{in}$ in dB	-3dB cutoff frequency
No serial resistance, input voltage = AC 1	Input voltage is the same, 0dB	319 kHz
Serial resistance with 50 $\Omega$ and input voltage = AC 1	Input voltage not changing, 0dB	1.11 Mhz
Serial resistance with 50 $\Omega$ and input voltage different than AC 1 (Voltage between $R_1$ and $R_2$ )	Input voltage changing, different than 0dB	1.11Mhz however the ratio is equal to 1

Table 3: Cutoff frequencies and Output/Input voltage ratio

### Introduction (Part 3):

In this part of the experiment, LM324 OPAMP is wanted to use and given the specific types of circuits, analyze which type of OPAMP circuit is it. The LM324 OPAMP is imported in LTSpice to use it in this experiment. First part of this experiment contains only resistors and the second part has a capacitor swapped with a resistor in the circuit.



## Methodology:

The shown circuit is created with the chosen values of  $R_1 = 0.5K \Omega$  and  $R_2 = 1.5K \Omega$ . The DC voltage values that are connected to OPAMP are +8V and -8V. The created circuit can be seen in Figure 3.1.

 


Figure 3.1: Desired OPAMP circuit with the chosen values of  $R_1$ ,  $R_2$ , and  $V_{cc}$ .

## Simulation:

Looking at the Input (Blue) and Output (Green) voltages on the Figure 3.2, it is seen that the input voltages are both inverted and amplified. This type of an OPAMP is called “Inverting OPAMP”. Input voltage value is 2V and the output voltage value is 6V which can be clearly seen in Figure 3.2.

 


Figure 3.2: Input and Output voltages of the circuit in Figure 3.1

In this step, I changed the sinusoidal voltage wave to square wave. With this change  $V_{in} = 1V$  and  $V_{out} = 3V$ , with the ratio  $R_2/R_1 = 3$ .

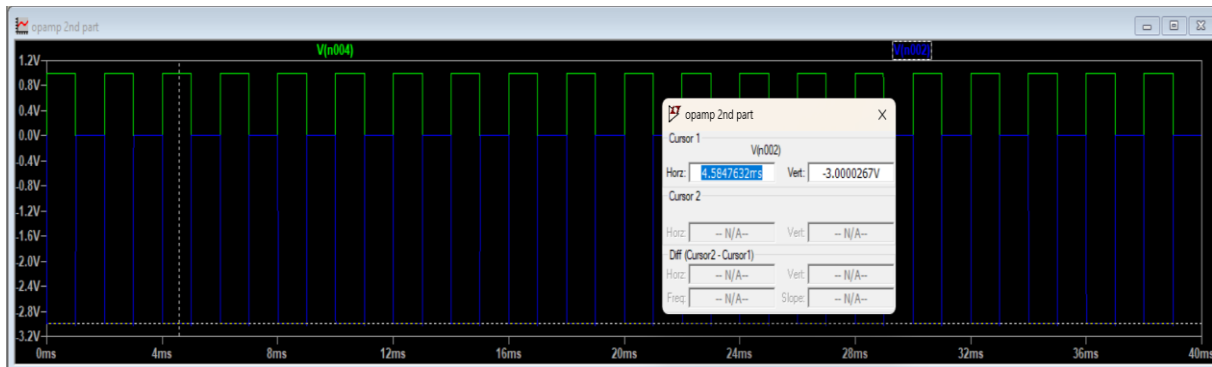


Figure 3.3:  $R_2/R_1 = 3$ , with square wave input voltage, output voltage = 3V

At the beginning of the Part 3, I choose the  $R_1$  and  $R_2$  values as  $R_2/R_1 = 3$ . Now, to find where does the OPAMP reaches its saturation point ( $-V_{cc} \leq V_{OUT} \leq V_{cc}$ ), I increased the  $R_2$  value gradually. At  $R_2 = 4K \Omega$ , the output voltage reached 7.93 V which is very close to the DC voltage (8V) that I also choose at the beginning. So, at  $R_2/R_1 = 8$ , OPAMP reached saturation point. Figure 3.4 shows the plot of the output voltage at saturation point.

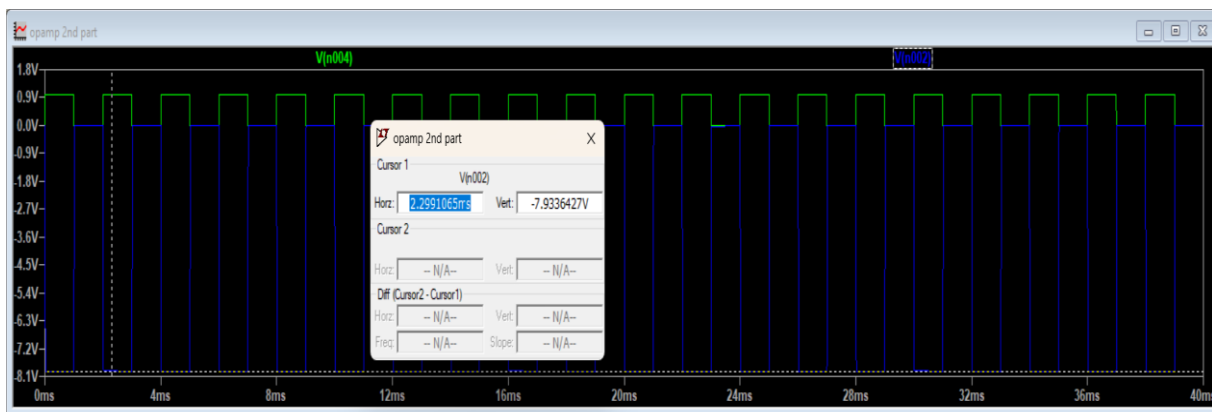


Figure 3.4:  $R_2/R_1 = 8$ , with square wave input voltage, output voltage = 7.93 V

Resistor Ratio	$R_2/R_1 = 3$	$R_2/R_1 = 8$
Output Voltage	$V_{out} = 3V$	$V_{out} = 7.93V$

Table 4:  $R_2/R_1$  ratio and corresponding output voltage value

For the last part of Part 3, I replace  $R_2$  with a 3nF capacitor and  $R_1$  with 8 K  $\Omega$  resistor. The new circuit now became a “Integrating OPAMP” circuit. Figure 3.6 shows the behavior of the circuit in Figure 3.5.

 


Figure 3.5: New OPAMP circuit with a capacitor

In order to see both +0.5V and -0.5V in square wave, I changed the initial value 0V to 0.5V and  $V_{on}$  from 1V to -0.5V. That way the expected output voltage is obtained with triangular waveforms (Figure 3.6). Also the output voltages min and max voltages are -7.99 V and 6.49 V.

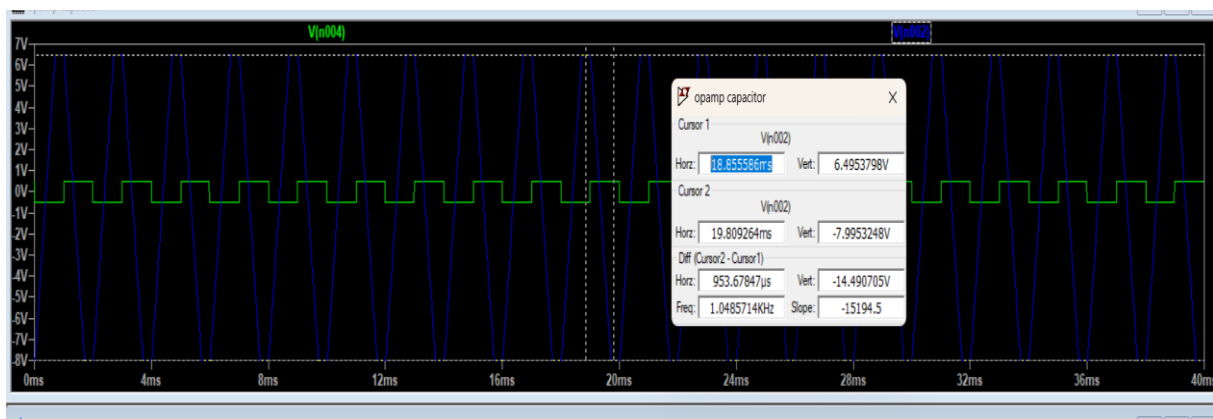


Figure 3.6: Plot of the output voltage in the circuit Figure 3.5

In the “Integrating OPAMP” circuit, if the input wave is in square waveform, output wave will be triangular due to the integration.

## Hardware Implementation

 


Figure 4.1: RL circuit in Figure 1.3

In software part, I used  $20\ \Omega$  resistor however, in lab, there is not any  $20\ \Omega$  resistor available therefore I choose  $22\ \Omega$  resistor while doing the hardware lab. I used  $10\ \mu\text{H}$  axial inductor that is available at the lab.

## Simulation:

For 8V sinusoidal 100 kHz input voltage, I get 2.22V as output voltage. (Figure 4.2)

 


Figure 4.2: RL circuit in Figure 1.3  
with frequency 100 kHz,  $V_{\text{out}} = 2.22\text{V}$

When I changed frequency value from 100kHz to 500kHz, output voltage increased to 5.80 V.

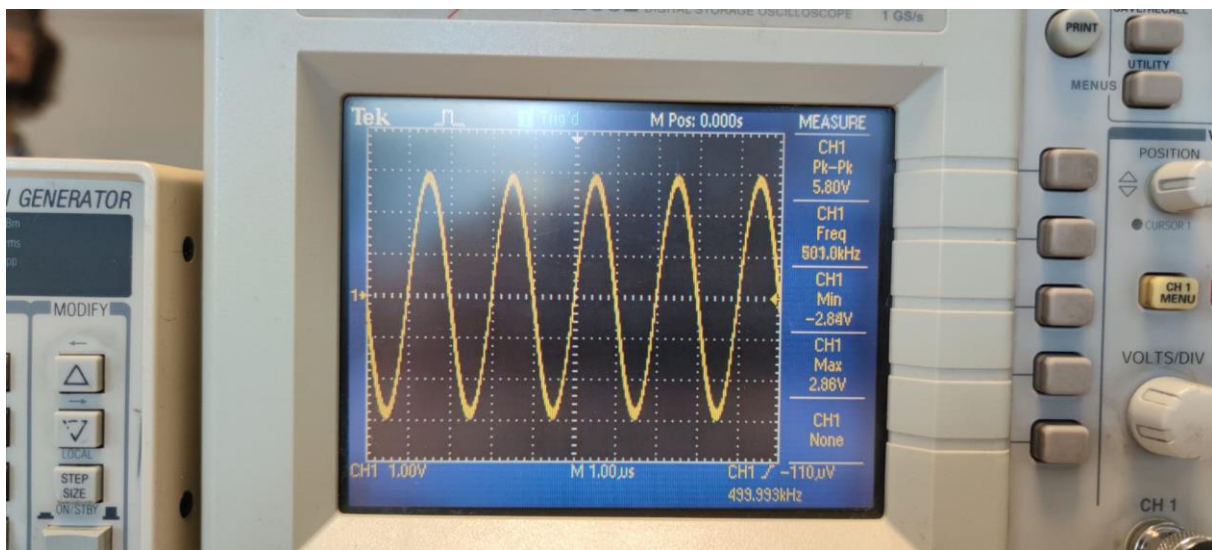


Figure 4.2: RL circuit in Figure 1.3  
with frequency 500 kHz,  $V_{out} = 5.80$  V

Lastly, when I changed the frequency value to 10kHz, output voltage decreased to 336 mV.

 


Figure 4.3: RL circuit in Figure 1.3  
with frequency 10 kHz,  $V_{out} = 336$  mV

	Hardware lab	Software lab
$f = 10\text{kHz}$	$V_{\text{out}} = 336\text{ mV}$	$V_{\text{out}} = 251\text{ mV}$
$f = 100\text{kHz}$	$V_{\text{out}} = 2.22\text{ V}$	$V_{\text{out}} = 2.4\text{ V}$
$f = 500\text{kHz}$	$V_{\text{out}} = 5.80\text{ V}$	$V_{\text{out}} = 6.7\text{ V}$

Table 5: frequency and output voltage relation for the designed RL circuit

As seen in the software lab, when frequency increases output voltage is also increasing there this circuit is a high-pass filter.

In this last part of the hardware lab, it is asked to create the OPAMP circuit in Figure 3.1 and the output voltage is observed. I used  $470\ \Omega$  as  $R_1$  and  $1.5\text{K}\ \Omega$  as  $R_2$ .

 


Figure 4.4: Waveform of the output voltage of the OPAMP circuit with  $V_{\text{in}} = 2\text{V}$   $1\text{kHz}$ , output voltage wave,  $V_{\text{outmax}} = 5.76\text{V}$  and  $V_{\text{outmin}} = -5.76\text{V}$

Software lab	Hardware Lab
$V_{\text{outmax}} = 6\text{V}$	$V_{\text{outmax}} = 5.76\text{V}$
$V_{\text{outmin}} = 6\text{V}$	$V_{\text{outmin}} = -5.76\text{V}$

Table 6: Output voltages for the OPAMP circuit, comparison of software and hardware lab datas

This circuit is an “Inverting Amplifier” because it amplifies the  $2\text{V}$  input voltage to  $5.76\text{V}$  output voltage and inverts the input voltage also (e.g  $V_{\text{in}} = 2\text{V}$  and  $V_{\text{out}} = -11.5\text{ V}$



 


Figure 4.5: Design of the OPAMP circuit with capacitor

For this circuit, because there is not any 3nF capacitor available, I used 3.3nF capacitor.

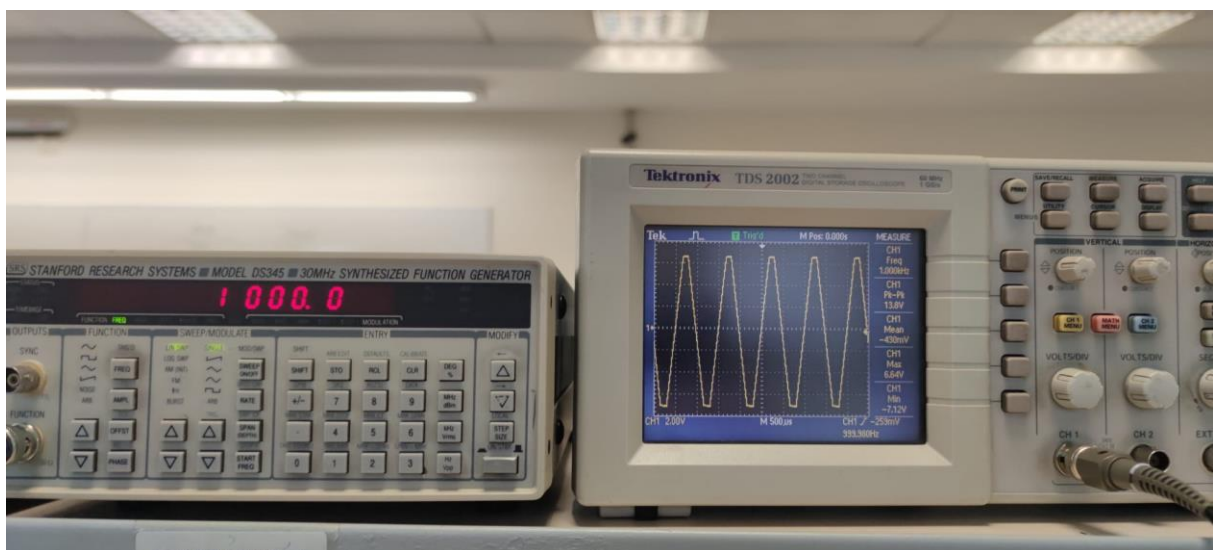


Figure 4.6: Output voltage waveform of OPAMP circuit with capacitor

Software Lab	Hardware Lab
$V_{outmax} = 6.49 \text{ V}$	$V_{outmax} = 6.64 \text{ V}$
$V_{outmin} = -7.99 \text{ V}$	$V_{outmin} = -7.12 \text{ V}$

Table 7: Output voltages for the OPAMP circuit with capacitor, comparison of software and hardware lab datas

This circuit acts like an “Integrating Amplifier” because we give square wave inputs and the outputs are triangular shaped waveforms. Also, the input voltage is amplified at the output of the OPAMP.

In Part 2 of the experiment, I find the following dB values at LTSpice:

$f = 10\text{kHz}$	-30.86 dB
$f = 100\text{kHz}$	-11.18 dB
$f = 500\text{kHz}$	-1.73 dB
$f = 351\text{kHz}$	-3 dB

Table 8: dB values for different frequencies

Figure 4.7 shows the datas taken from the hardware lab.

 


Figure 4.7: dB scale plot for RL circuit

Comparing Table 8 and Figure 4.7, at frequencies 10kHz and 100kHz, datas are very close to each other however, at 500kHz, there is approximately 1 dB difference. The difference may occurred due to the experimenter’s insensitivity or it also may cause from the signal generator in labs.



**Conclusion:**

The first 2 part of the experiment mainly purposes to examine the time and frequency domain of R and RL circuits. The third part of the assignment relies on the input and output voltage ratios of the OPAMP circuits.

Through experiment, some errors happened. The reason for these errors in hardware labs are caused by the experiment materials, for example in the lab there is not 3nF capacitor and some desired resistor values, therefore experimenter used the nearest values for these materials. Also, some errors caused by the experimenter because it is not sensitive enough while measuring the datas in both software and hardware labs. Nevertheless, there are slight differences between software and hardware lab datas.