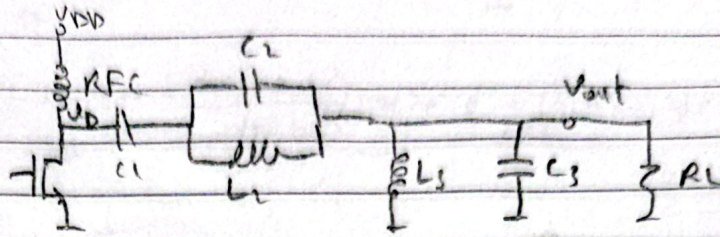


Question 1)



$$a) R_{series} = \frac{\omega_0 L_2}{Q_1} = \frac{2\pi \times 300 \text{ MHz} \times 50 \text{ nH}}{125} = \boxed{0.75 \Omega} \text{ equivalent series resistance of } L_2$$

$$R_{parallel} = Q_2 \times \omega_0 L_1 = \boxed{11,780.97 \Omega \approx 11,781 \Omega} \text{ equivalent parallel resistance of } L_1$$

$$b) R_{series} = \frac{\omega_0 L_1}{Q_3} = \frac{2\pi \times 100 \text{ MHz} \times 22 \text{ nH}}{90} = \boxed{0.154 \Omega} \text{ eq. series resistance of } L_1$$

$$R_{parallel} = Q_1 \times \omega_0 L_2 = \boxed{1,244 \Omega} \text{ eq. parallel resistance of } L_2$$

c) Resonate at  $f_0 = 300 \text{ MHz}$ 

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow C_2 = \frac{1}{L_2 \times \omega_0^2} = \boxed{5.63 \text{ pF}}$$

d) Resonate at  $f_0 = 100 \text{ MHz}$ 

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow C_3 = \frac{1}{L_3 \times \omega_0^2} = \boxed{115.14 \text{ pF}}$$

$$e) X_C = \frac{1}{C \cdot \omega_0} = \frac{R_L}{20} = 2.5 \Omega$$

$$C_1 = \frac{1}{2.5 \times 2\pi \times 100 \text{ MHz}} = \boxed{636.62 \text{ pF}}$$

$$X_L = \omega_0 L = 15 R_L = 750 \Omega$$

$$L_{RFC} = \frac{750}{\omega_0} = \frac{750}{2\pi \times 100 \text{ MHz}} = 1.19 \mu\text{H}$$



$$f) R_2 + (R_L // R_{sp}) = \frac{9}{8} \frac{(V_{DD} - V_{SAT})}{I_1}$$

$$\left. \begin{array}{l} R_2 = 0.75 \Omega \\ R_L = 50 \Omega \\ R_{sp} = 1244 \Omega \end{array} \right\} R_2 + (R_L // R_{sp}) = 0.75 + \frac{50 \times 1244}{50 + 1244} = 48.82 \Omega$$

$$I_1 = \frac{I_{max}}{2\pi(1 - \cos \frac{\alpha}{2})} (1 - \sin \alpha) = \boxed{\frac{I_{max}}{2}}$$

$$\hookrightarrow 48.82 = \frac{9}{8} \frac{(28-1)}{0.5 I_{max}} \Rightarrow 0.5 I_{max} = \frac{9}{8} \cdot \frac{27}{48.82}$$

$$\Rightarrow \boxed{I_{max} = 1.244 \text{ A}}$$

$$g) \sin \delta = \frac{3\pi \cdot (28-1)}{8 \times 11.781 \times 1.244} = 2.17 \times 10^{-3} \Rightarrow \boxed{\delta = 0.124^\circ}$$

$$\alpha = \pi + 0.124^\circ \Rightarrow \alpha = 180.124^\circ = 3.1438 \text{ rad} \quad (\alpha \approx \pi)$$

$$h) I_0 = \frac{I_{max}}{2\pi} \frac{2 \sin \frac{\alpha}{2} - \cos \frac{\alpha}{2}}{1 - \cos \frac{\alpha}{2}} = \boxed{0.396 \text{ A}} \quad \text{where } \alpha = \pi + \delta$$

$$i) I_1 = \frac{I_{max}}{2} = 0.622 \text{ A}$$

$$R_{opt} = \frac{9}{8} V_{DD} \cdot \frac{1}{I_1} = 48.82 \Omega$$

$$P_{out} = \left(\frac{9}{8} V_{DD}\right)^2 \cdot \frac{1}{2} \cdot \frac{1}{R_{opt}} = 9.45 \text{ W}$$

$$P_{RL} = \frac{V_p^2}{2} \cdot \frac{1}{R_L} \Rightarrow V_p = I_1 \times (R_L // R_{sp}) = 29.9 \text{ V}$$


$$\hookrightarrow P_{RL} = \frac{29.9^2}{2} \cdot \frac{1}{50} = \boxed{8.94 \text{ W}} \quad \left. \vphantom{\frac{29.9^2}{2} \cdot \frac{1}{50}} \right\} \eta = 80.63\%$$

$$j) P_{DC} = V_{DD} \times I_0 = 28 \times 0.396 = \boxed{11.088 \text{ W}}$$

$\eta$  is higher than class B, which is at max. 78.5%



Question 2)

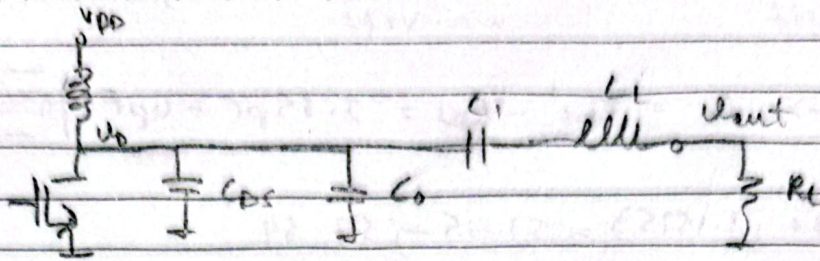

$f_0 = 100 \text{ MHz}$      $C_{gs} = 4 \text{ pF}$      $R_L = 50 \Omega$      $V_{DD} = 24 \text{ V}$

a)  $X_L = 15 R_L$  at  $f_0$

$X_L = 750 \Omega$

$X_L = \omega_0 L \Rightarrow L_{RFC} = \frac{X_L}{\omega_0} = \frac{750}{2\pi \times 100 \text{ MHz}} = 1.19 \mu\text{H}$

1008AF - 132 X-RC inductor is chosen, its inductance is  $1.3 \mu\text{H}$   
reactance is  $817 \Omega$ , where as chosen resistance value is  $750 \Omega$

b)  $R_{DC}$  is  $0.11 \Omega$ , from the datasheet.

c)  $\frac{\omega_0 L_1}{R_L} = Q \Rightarrow L_1 = \frac{Q \cdot R_L}{2\pi f_0}$   
for  $Q=5 \Rightarrow L_1 = 398 \text{ nH}$   
for  $Q=10 \Rightarrow L_1 = 796 \text{ nH}$

2929SQ - 501 - EL inductor is chosen, which has a value of  $500 \text{ nH @ } 50 \text{ MHz}$

d) Inductor's  $Q$  is  $180$  @  $50 \text{ MHz}$ . Using that information:

$\frac{\omega_0 L_1}{R_1} = Q \Rightarrow R_1 = \frac{\omega_0 L_1}{Q} = \frac{2\pi \times 100 \text{ MHz} \times 500 \text{ nH}}{180} = 1.75 \Omega$

e)  $R_{\text{load effective}} = R_1 + R_L = 1.75 \Omega$

$V_{eff} = V_{DD} - I_{DC} R_{DC} = 24 - 0.11 I_{DC}$

$R_{\text{load eff}} = \frac{V_{eff}}{I_{DC}} \cdot \frac{8}{\pi^2 - 4} \Rightarrow I_{DC} = \frac{V_{eff}}{R_{\text{load eff}}} \cdot \frac{8}{\pi^2 - 4}$

$\Rightarrow I_{DC} = 0.267 \text{ A}$  using the solve function of the calculator.



$$f) \omega C_{DS}' = \frac{I_{DC}}{\pi \cdot V_{eff}} \Rightarrow C_{DS}' = \frac{I_{DC}}{\omega \pi \cdot V_{eff}} = 5.65 \text{ pF}$$

$$C_{DS}' = C_{DS} + C_0 \Rightarrow C_0 = C_{DS}' - C_{DS} = 5.65 \text{ pF} - 4 \text{ pF} = \boxed{1.65 \text{ pF}}$$

$$g) -Z_L = R_{load} (1 + j 1.1575) = 51.75 + j 59.64$$

$$\text{Output reactance} = \omega_0 L_1 - \frac{1}{\omega_0 C_1} = 59.64$$

$\omega_0 = 214.16$

$$\Rightarrow \omega_0 C_1 = \frac{1}{254.52} \Rightarrow C_1 = \frac{1}{\omega_0 \times 254.52} = \boxed{6.25 \text{ pF}}$$

$$h) P_{out} = V_{eff} \times I_{DC} = 6.4 \text{ W}$$

But power delivered to load is different:

$$P_L = P_{out} \times \frac{R_L}{R_L + R_1} = \boxed{6.18 \text{ W}} \quad \left| \quad \eta = 96.44\% \right|$$

$$i) P_{DC} = V_{DD} \times I_{DC} = 6.408 \text{ W}$$

$$j) V_p = 3.56 \times V_{eff} = \boxed{85.34 \text{ V}}$$

$$k) I_p = 2.86 \times I_{DC} = \boxed{0.764 \text{ A}}$$