

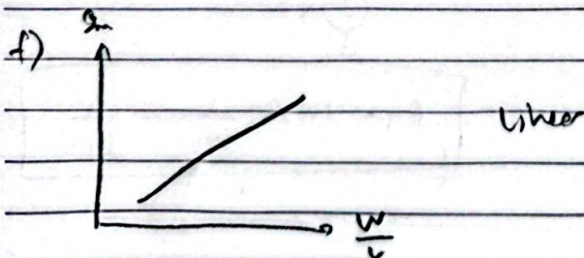
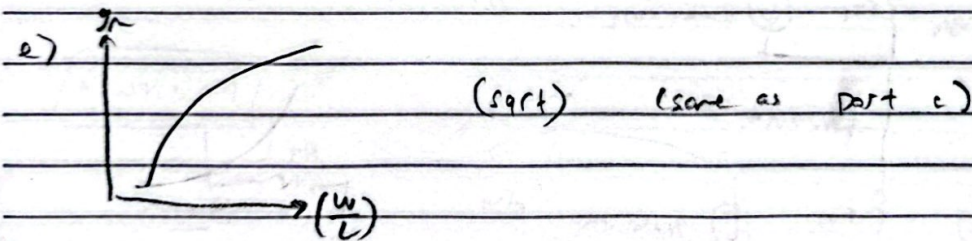
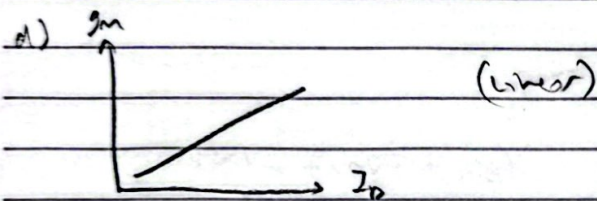
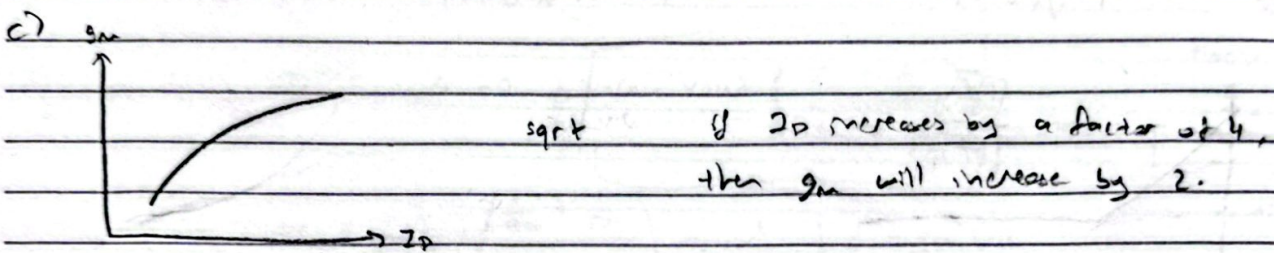
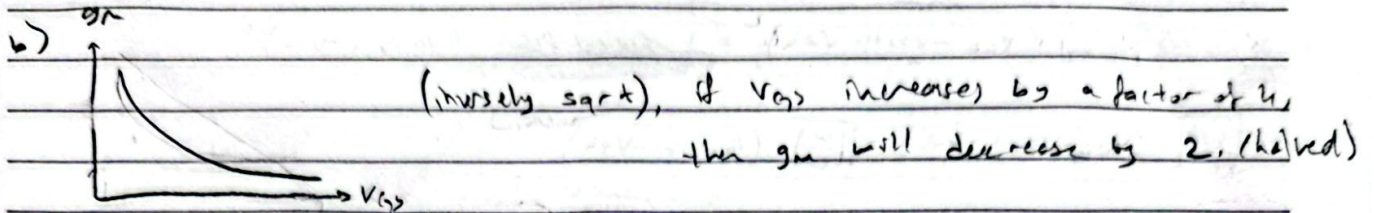
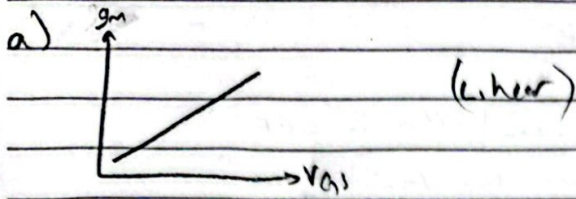

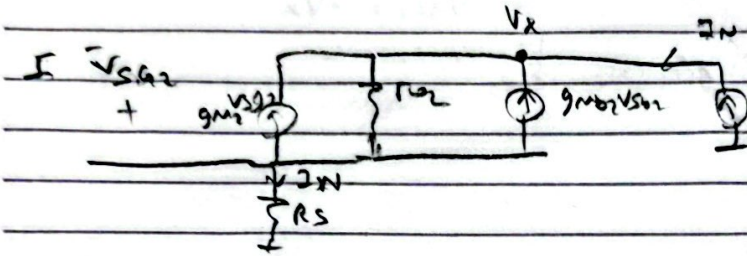
$$1) g_m = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right) \cdot I_D} = \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_{th}) = \frac{2 I_D}{V_{GS} - V_{th}}$$



2) Norton eq. ???
 a) couldn't figured out
 how to show M_1
 as a Norton eq.
 circuit. I solve by
 a different
 approach

M_1 don't suffer from body
 effect

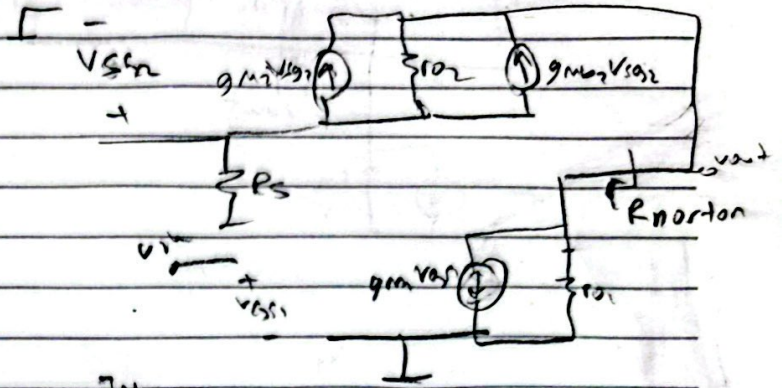

$$V_{S2} = I_N R_S$$

$$V_{SSN} = I_N R_S$$


$$V_{S2} = V_{S2}$$

at V_X :

$$-I_N + \frac{V_X - V_{S2}}{r_{o2}} - g_{m2} V_{S2} - g_{m2} V_{S2} = 0$$

$$I_N \left[1 + R_S \left(\frac{1}{r_{o2}} + g_{m2} + g_{m2} \right) \right] = \frac{V_X}{r_{o2}}$$
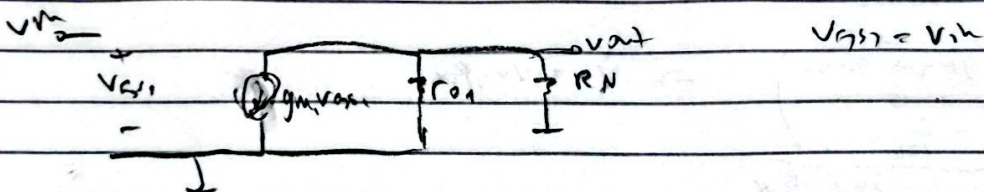
$$\frac{V_X}{I_N} = r_{o2} \left[1 + R_S \left(\frac{1}{r_{o2}} + g_{m2} + g_{m2} \right) \right] = R_N$$




at v_{out} :

$$\frac{v_{out}}{R_N} + \frac{v_{out}}{r_{o1}} + g_{m1} V_{GS1} = 0 \Rightarrow v_{out} \left(\frac{1}{R_N} + \frac{1}{r_{o1}} \right) = -g_{m1} V_{GS1}$$

$$\boxed{\frac{v_{out}}{v_{in}} = - \frac{g_{m1}}{\left(\frac{1}{R_N} + \frac{1}{r_{o1}} \right)}}$$

3)

c)

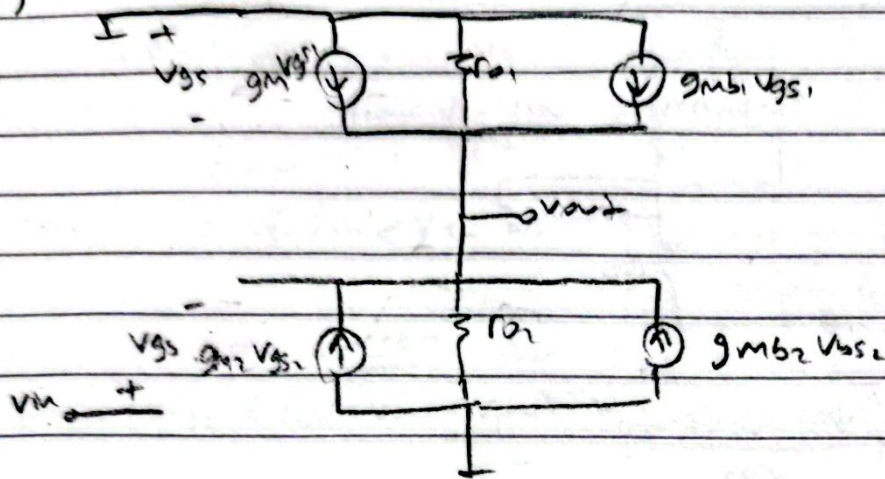

$$V_{gs1} = -v_{out} = V_{bs1}$$

$$V_{gs2} = V_{in} - v_{out}$$

$$V_{b12} = V_{DD} - v_{out}$$

vout:

$$\frac{v_{out}}{r_{o1}} = \frac{v_{out}}{r_{o2}} + v_{out} (g_{m2} + g_{mb2}) + (v_{out} - V_{th}) g_{m1} + (v_{out} - V_{DD}) g_{mb1}$$

$$v_{out} \left(\frac{1}{r_{o1}} + \frac{1}{r_{o2}} + g_{m2} + g_{mb2} + g_{m1} + g_{mb1} \right) = V_{in} g_{m1} + V_{DD} g_{mb1}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{V_{th}} \left(\frac{V_{in} g_{m1} + V_{DD} g_{mb1}}{\frac{1}{r_{o1}} + \frac{1}{r_{o2}} + g_{m1} + g_{m2} + g_{mb1} + g_{mb2}} \right)$$

why is there an offset term in the gain equation?

4) $V_{D2} = V_{G2} = V_{DD} \Rightarrow M_2$ always SAT

For M_1 $V_{D1} = V_{out}$, $V_{G1} = V_D$, $V_{S1} = V_{in}$

$V_{DS} = V_{out} - V_{in}$ $V_{GS} = V_D - V_{in}$

Assume OFF state

$V_{GS} < V_{th} \Rightarrow V_D - V_{in} < V_{th} \Rightarrow$ $V_{in} > V_D - V_{th}$ M_1 is OFF


SO $V_{out} = V_{DD} - V_{th}$

Now assume M_1 is SAT, then $I_{D2} = I_{D1}$

~~$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{out} - V_{th})^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_D - V_{in} - V_{th})^2$~~


$\Rightarrow \sqrt{\left(\frac{W}{L}\right)_2} \cdot (V_{DD} - V_{out} - V_{th}) = \sqrt{\left(\frac{W}{L}\right)_1} \cdot (V_D - V_{in} - V_{th})$

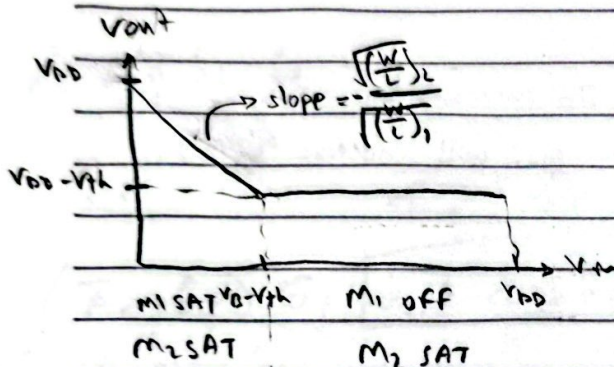$\sqrt{\left(\frac{W}{L}\right)_2} V_{out} = \sqrt{\left(\frac{W}{L}\right)_1} (V_{in} - V_D) + V_{th} \left(\sqrt{\left(\frac{W}{L}\right)_1} - \sqrt{\left(\frac{W}{L}\right)_2} \right) + V_{DD} \sqrt{\left(\frac{W}{L}\right)_2}$



$V_{GS2} = -V_{out} = V_{GS2}$

$V_{GS1} = -V_{in} = V_{GS1}$

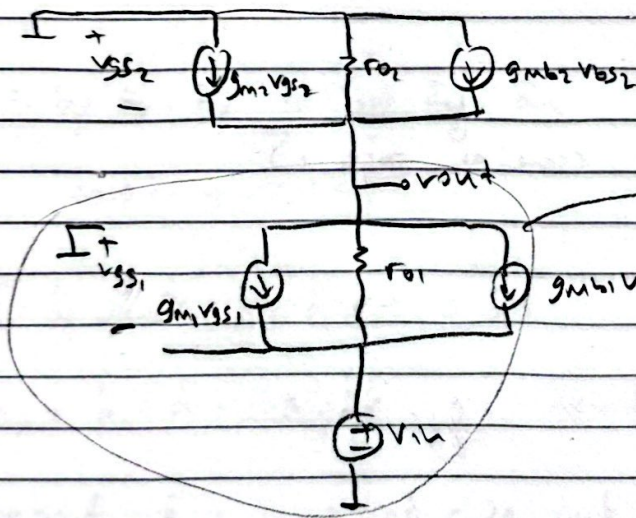

M_2 circuit

$R_T = r_{o1} \parallel \frac{1}{g_{m1}} \parallel \frac{1}{g_{mb1}}$

KCL at V_{out} :


$\frac{V_{out}}{r_{o2}} + V_{out} (g_{m2} + g_{mb2}) + \frac{V_{out} - V_{th}}{r_{o1}} - V_{th} (g_{m1} + g_{mb1}) = 0$

$= V_{out} \left(\frac{1}{r_{o2}} + g_{m2} + g_{mb2} + \frac{1}{r_{o1}} \right) = V_{th} \left(\frac{1}{r_{o1}} + g_{m1} + g_{mb1} \right)$

$\frac{V_{out}}{V_{th}} = \frac{\frac{1}{r_{o1}} + g_{m1} + g_{mb1}}{\frac{1}{r_{o1}} + \frac{1}{r_{o2}} + g_{m2} + g_{mb2}}$

5)

b)

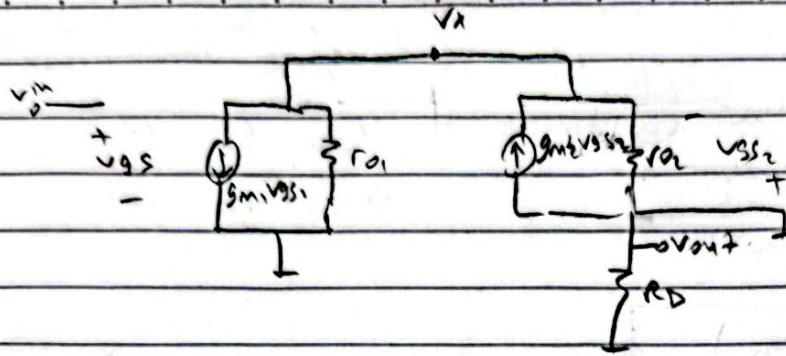

$$V_{GS2} = -V_x$$

$$V_{GS1} = V_{in}$$

KCL at V_x :

$$\frac{V_x}{r_{o1}} + g_{m1}V_{in} + g_{m2}V_x + \frac{V_x - v_{out}}{r_{o2}} = 0$$

$$V_x \left(\frac{1}{r_{o1}} + \frac{1}{r_{o2}} + g_{m2} \right) + g_{m1}V_{in} - \frac{v_{out}}{r_{o2}} = 0$$

KCL at v_{out} :

$$\frac{v_{out}}{R_D} + \frac{v_{out} - V_x}{r_{o2}} - g_{m2}V_x = 0 \Rightarrow V_x = v_{out} \left(\frac{\frac{1}{R_D} + \frac{1}{r_{o2}}}{g_{m2} + \frac{1}{r_{o2}}} \right)$$

$$\Rightarrow v_{out} \left[\left(\frac{1}{r_{o2}} + g_{m2} + \frac{1}{r_{o1}} \right) \cdot \left(\frac{\frac{1}{R_D} + \frac{1}{r_{o2}}}{g_{m2} + \frac{1}{r_{o2}}} \right) - \frac{1}{r_{o2}} \right] = -g_{m1}V_{in}$$

$$\frac{v_{out}}{V_{in}} = - \frac{g_{m1}}{\left(\left(\frac{1}{r_{o1}} + g_{m2} + \frac{1}{r_{o2}} \right) \cdot \left(\frac{\frac{1}{R_D} + \frac{1}{r_{o2}}}{g_{m2} + \frac{1}{r_{o2}}} \right) - \frac{1}{r_{o2}} \right)}$$

a)