

**EE419/519 Homework Assignment #2**

"I completed this homework assignment independently."

**Introduction:**

The purpose of this homework is designing a Buck converter which takes 320V as input voltage and give 3.3V as output voltage with  $R_L=5\Omega$ .

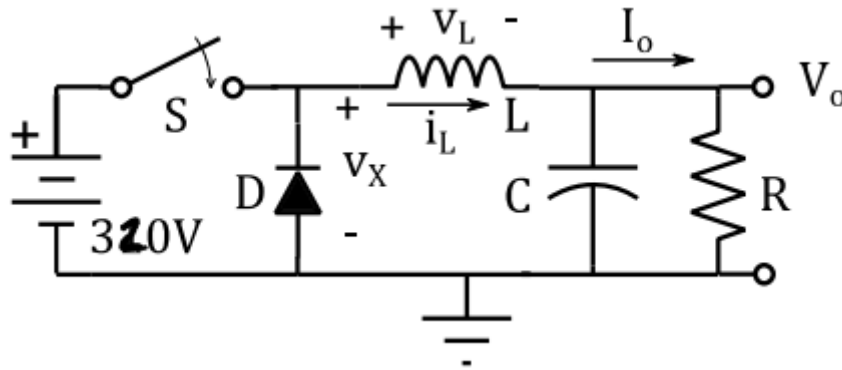


Fig. 1: Circuit Diagram

**Design Specifications:**

- a) Switching frequency is calculated as 30kHz. The formula for the duty cycle is given below for continuous mode operation.

$$V_o = V_D * D$$

Using this equation, D (duty cycle) is found as 0.01, so  $t_{ON}=0.33\mu s$ , where  $T_s=33.3\mu s$ .

- b) In order to find the minimum L value, I need to consider where  $i_L(0)=0$  and  $I_o \geq I_{OB}$ . The formulas are given below.

$$I_o = \frac{V_o}{R} = \frac{3.3V}{5\Omega} = 0.66A$$

$$I_{OB} = \frac{T_s V_d}{2L} * (D - D^2)$$

$$i_{lpeak} = 2I_{OB} = 0.33A$$

Using these equation, minimum L value is calculated as 79.92μH. Because it is written choose at least twice this value, 160μH value is chosen.

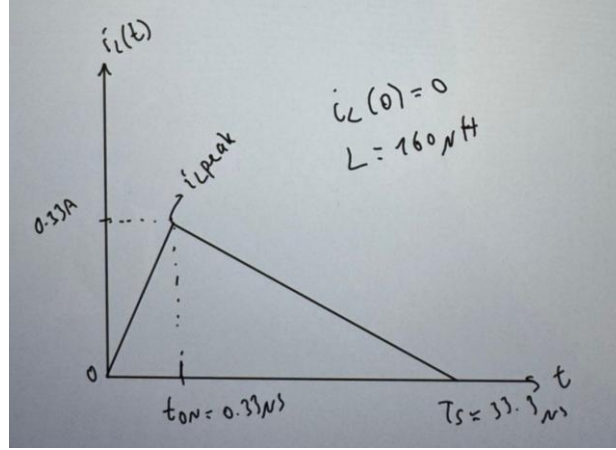


Fig. 2:  $i_L(t)$  graph with  $i_L(0)=0$  (boundary case)

- c) To obtain 15mV output ripple with zero ESR, following formula is going to be used to determine the capacitor value.

$$\Delta V_O = \frac{1}{8C} * \frac{T_s^2 V_O}{L} * (1 - D)$$

From this equation, C value is calculated as 188μF.

Now, taking into consideration the ESR, following formula will give us the output voltage ripple due to ESR of the capacitor.

$$\Delta V_{ESR} = \frac{8LC}{(1 - D)T_s \frac{V_O}{L} R_{ESR}}$$

From this equation, peak-to-peak output voltage ripple due to ESR is calculated as 0.1V.

- d) I choose L value as 10μH for this case. Using the formula below,  $V_O$  value will be calculated.

$$V_O = \frac{D^2}{D^2 + \frac{I_O}{4 * I_{OBMAX}}} * V_d \quad \text{where } I_{OBMAX} = \frac{T_s V_d}{8L}$$

$V_O$  value is calculated as 12.8V when D is preserved. The new  $I_O$  value is 2.56A where  $I_{OB}=5.27A$ . It is seen that the Buck converter is in discontinuous mode.  $i_{Lpeak}$  value is calculated as 20.45A, where  $\Delta_1$  value is calculated as 0.48. The formula for  $\Delta_1$  and  $i_{Lpeak}$  are given below for discontinuous mode.

$$\Delta_1 = \frac{I_O}{4 * I_{OBmax} * D}, \text{ where } I_{OBmax} = \frac{T_s V_d}{L}$$

$$i_{Lpeak} = \frac{V_o \Delta_1 T_s}{L}$$

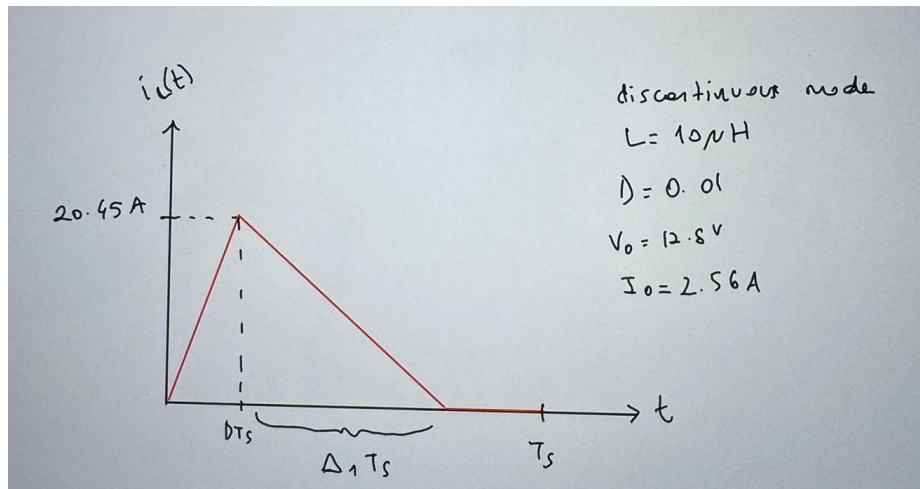


Fig. 3:  $i_L(t)$  graph when  $L=10\mu H$ ,  $V_o=12.8V$ , and  $D=0.01$  in discontinuous mode

- e) Again using the equation above, the new duty cycle  $D$  is calculated as  $3.59 \times 10^{-3}$ , so  $t_{ON}=0.119\mu s$ .  $I_o$  value is the same as the initial value which is  $0.66A$ . The corresponding  $\Delta_1$  value is calculated as  $0.69$ .  $i_{Lpeak}$  value is calculated as  $7.58A$ .

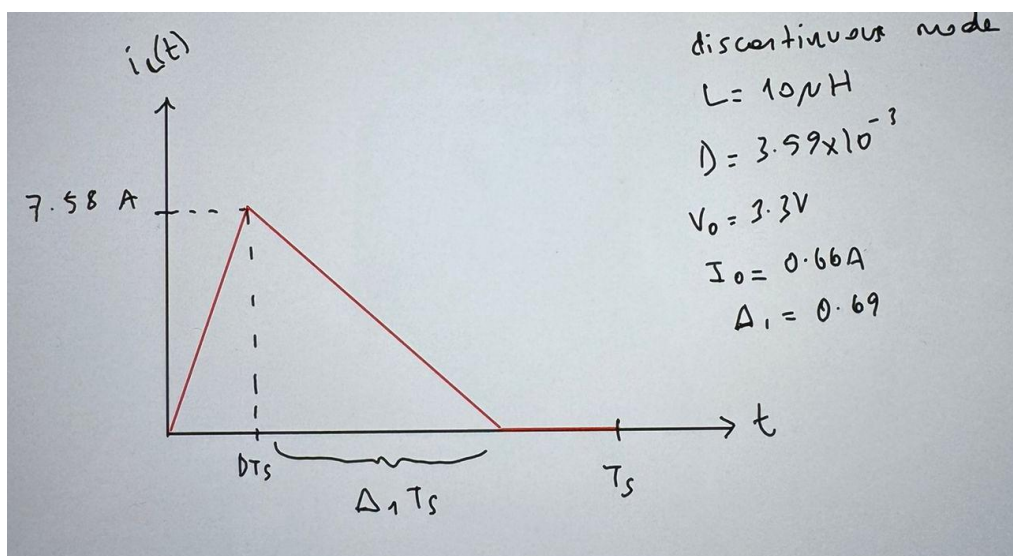


Fig. 4:  $D=3.59 \times 10^{-3}$ ,  $L=10\mu H$ , and  $V_o=3.3V$  in discontinuous mode  $i_L(t)$  graph

- f) Figure below shows the switching period value measured from the inductor current  $i_L(t)$ .

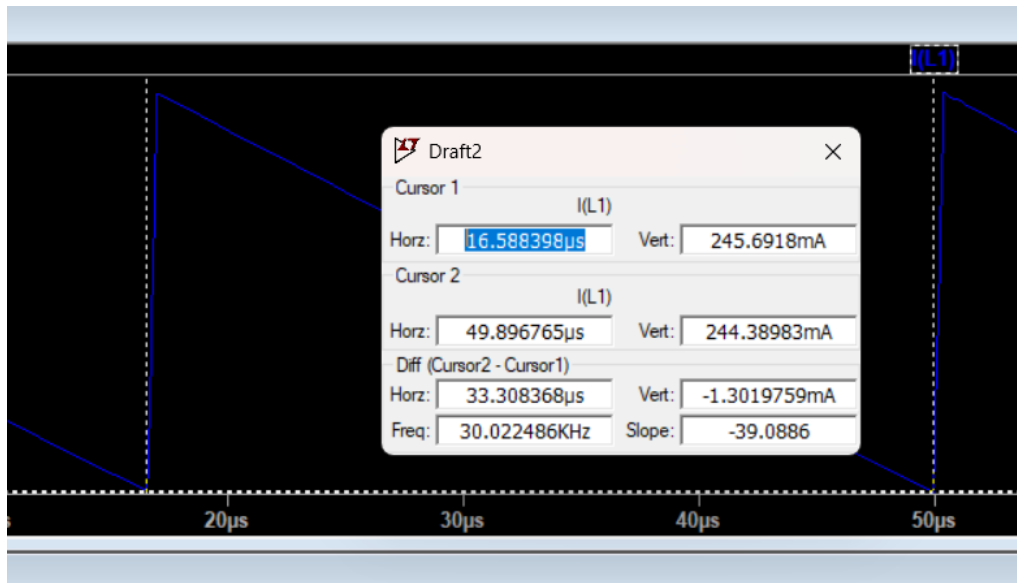


Fig. 5:  $T_s$  value

As calculated in the beginning, switching period is measured as 33.3 $\mu$ s. Figure below shows the waveform of the inductor current graph.

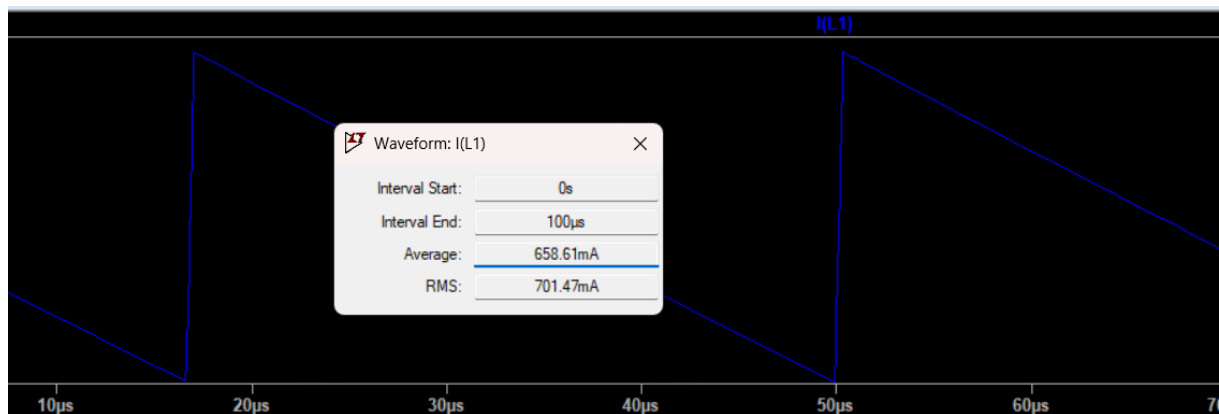


Fig. 6: Inductor current

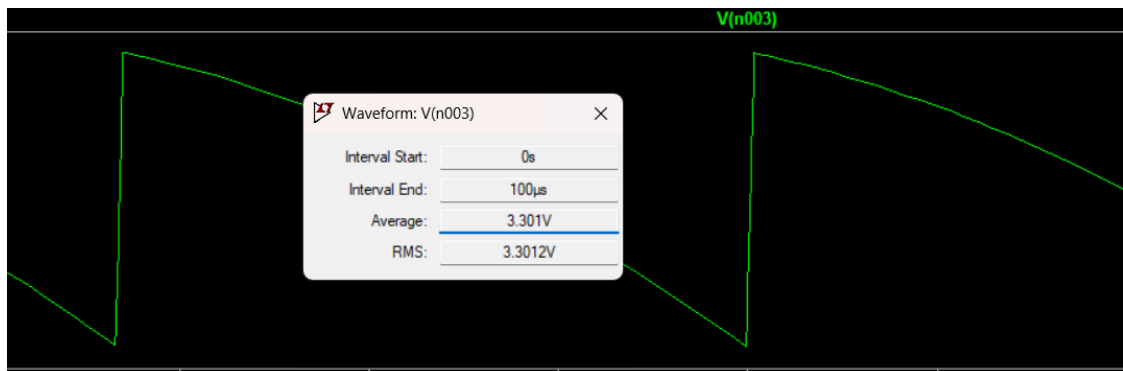


Fig. 7: Output voltage graph with value  $V_o=3.3V$

In the beginning, the  $t_{ON}$  value is calculated as  $0.33\mu s$ , however, due the voltage drop across the diode, some adjustments are done and finally  $t_{ON}=0.37\mu s$  value is used in the circuit.

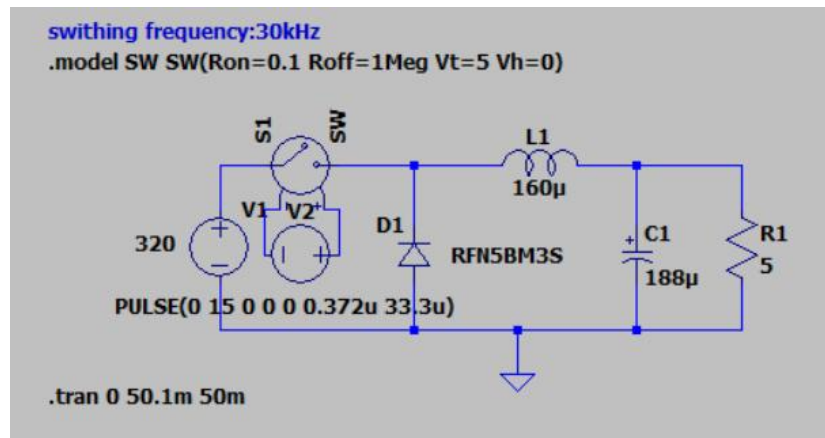


Fig. 8: Desinged Circuit

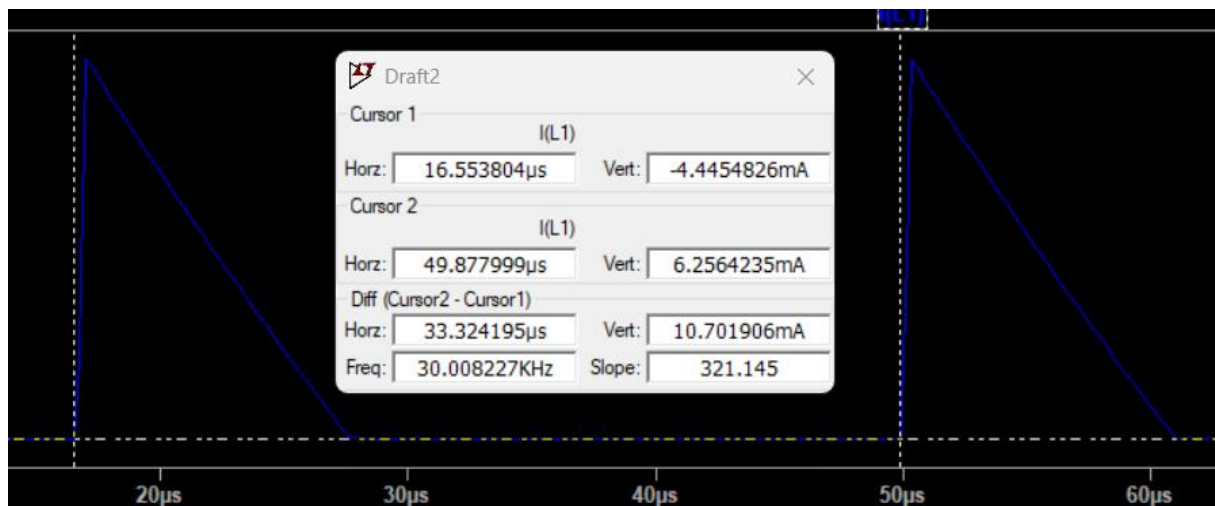


Fig. 9: Switching period in discontinuous mode

g) As seen from Fig. 7, switching period is still  $33.3\mu s$ .

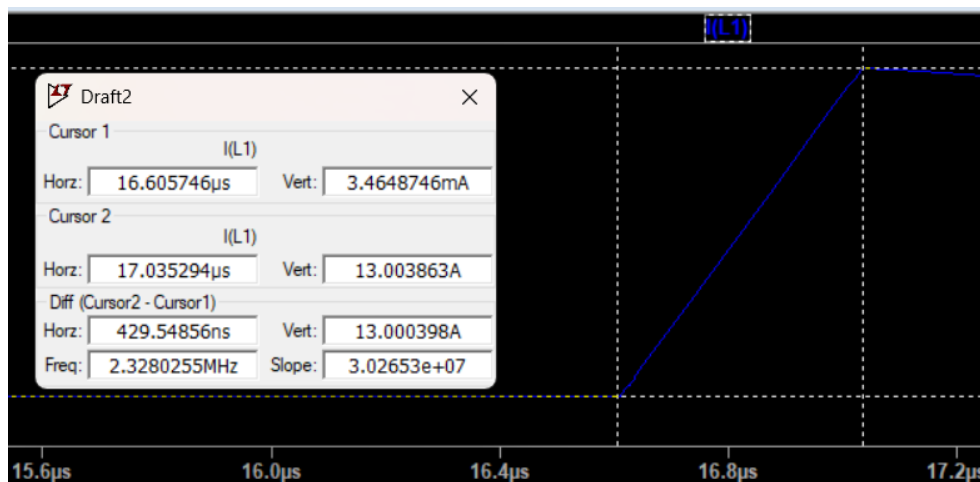


Fig. 10:  $t_{ON}=0.429\mu s$

The duty cycle value is calculated as  $D=0.012$ , which is nearly the same value initially calculated (initially  $D=0.010$ ).

In d),  $I_O$  value is calculated as 2.56A, whereas in the simulation,  $I_O$  value is measured as 2.1A. The difference is 0.4A and it is due to the voltage drop across the diode and equivalent series resistance of the capacitor.

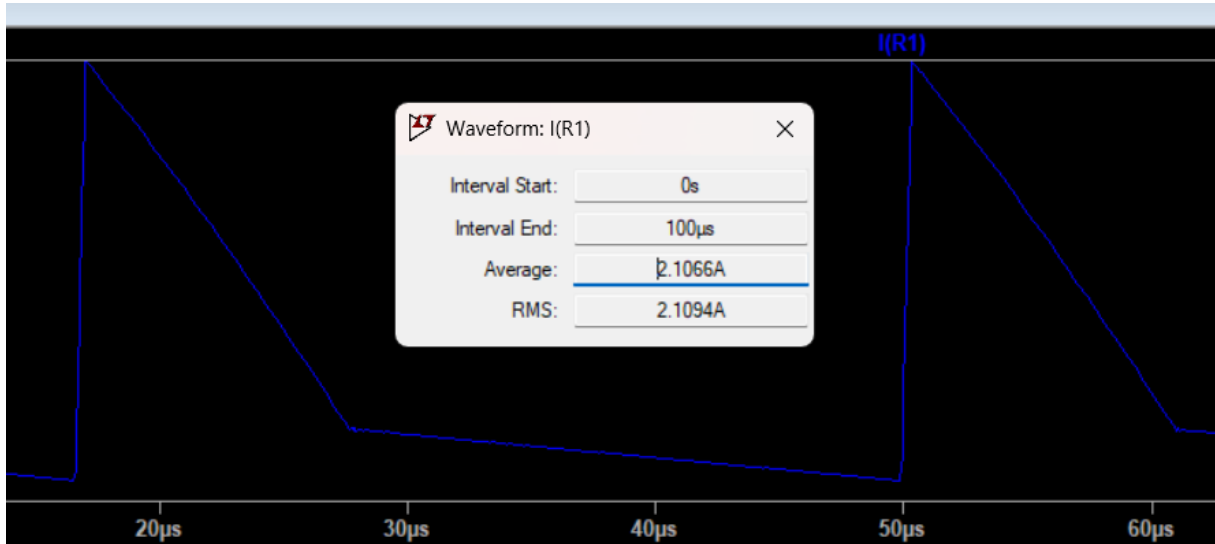


Fig. 12:  $I_O=2.1A$  in discontinuous mode

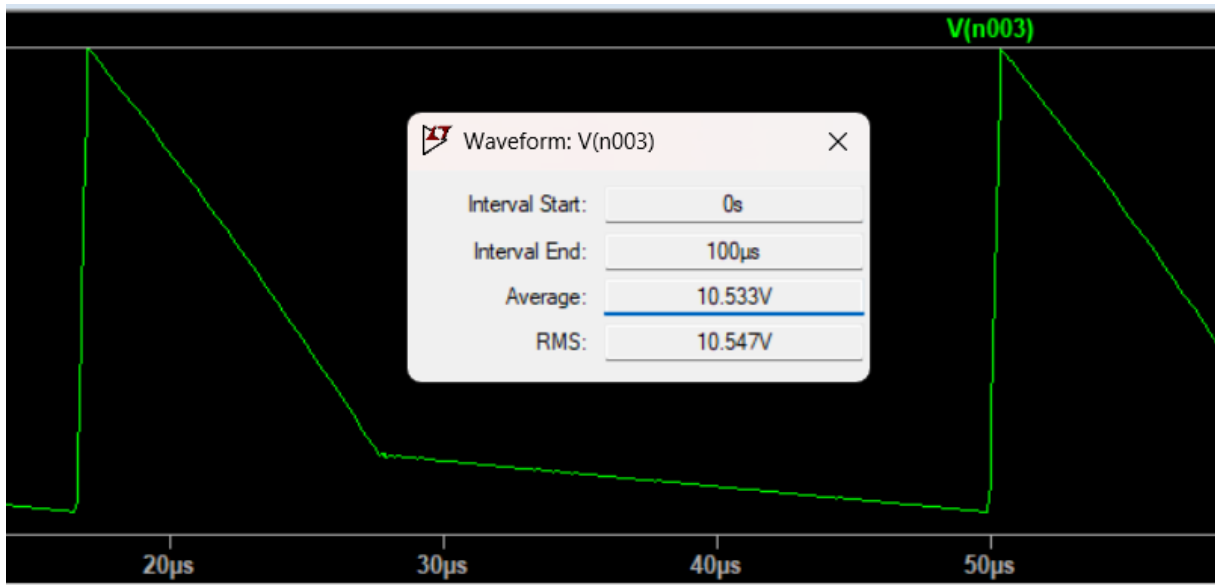


Fig. 13: Output voltage in discontinuous mode

In d), output voltage is calculated as 12.8V, however in the simulation, the measured value of it is 10.5V, again this is related to the difference in  $I_O$  values. The  $i_{L\text{peak}}$  value is

calculated as 20.45A in d) whereas in the simulation, the peak inductor current value is measured as 12.98A.

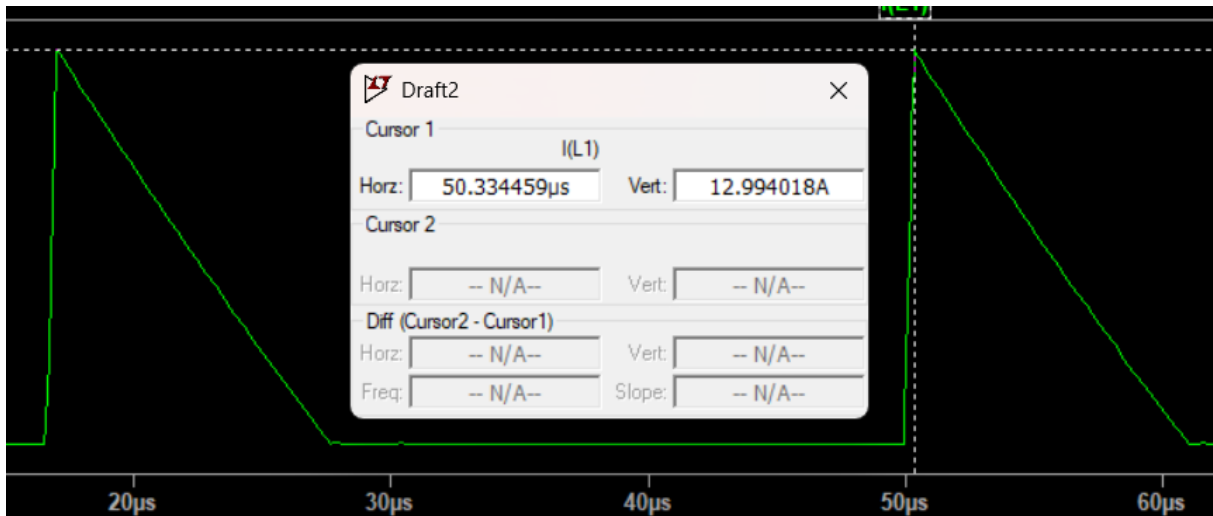


Fig. 14:  $i_{Lpeak}$  value for discontinuous mode and  $D=0.01$

- h) In e),  $D$  is calculated as  $3.59 \cdot 10^{-3}$ , and  $t_{ON}=0.119 \mu s$ . In the simulation, a slight adjustment was made to get 3.3V at the output. The  $t_{ON}$  value is determined as  $0.1238 \mu s$  and corresponding  $D$  value is  $3.72 \cdot 10^{-3}$ .

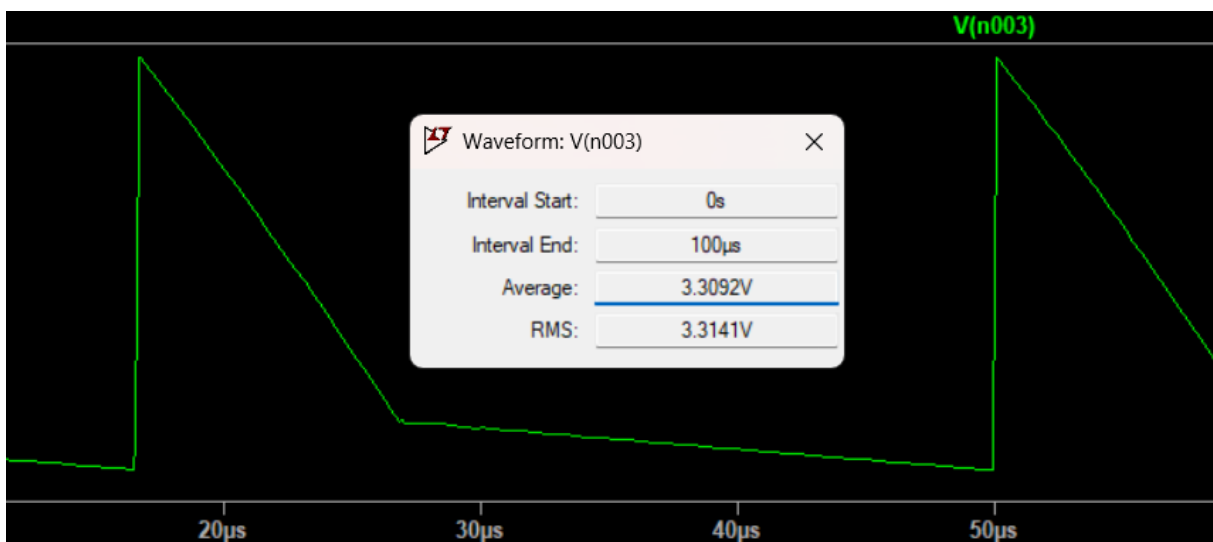


Fig. 15: 3.3V output voltage with  $L=10 \mu H$  in discontinuous mode

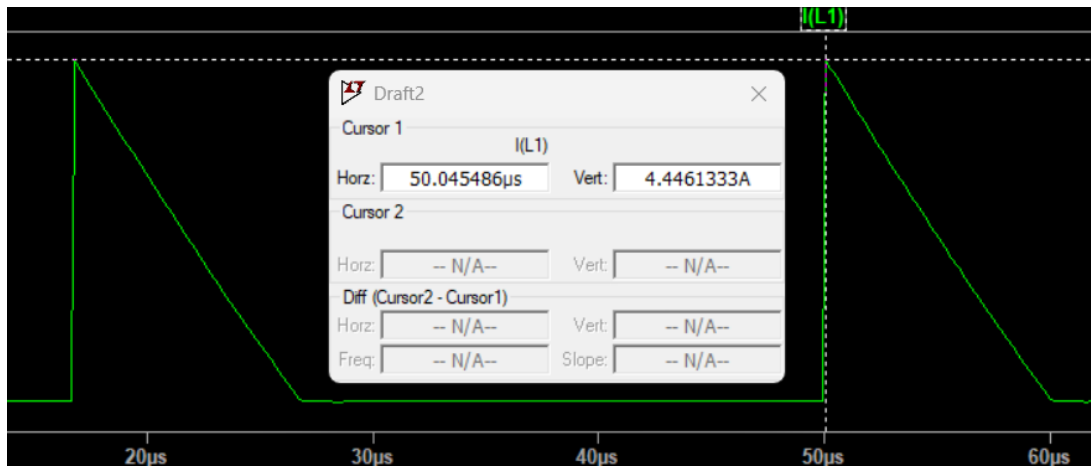


Fig. 16: Inductor current graph  $i_L(t)$  with  $V_o=3.3V$  in discontinuous mode

In e), peak inductor current value is calculated as 7.58A, however in the simulation, the value is measured as 4.45A. The difference is due to the voltage drop across the components and ESR of the capacitor.

- i) When both Diode and Switch are OFF, the diode voltage  $v_x(t)$  starts to oscillate until the period is completed. Figure below shows that the frequency of the sinusoidal is measured as 8.01Mhz.

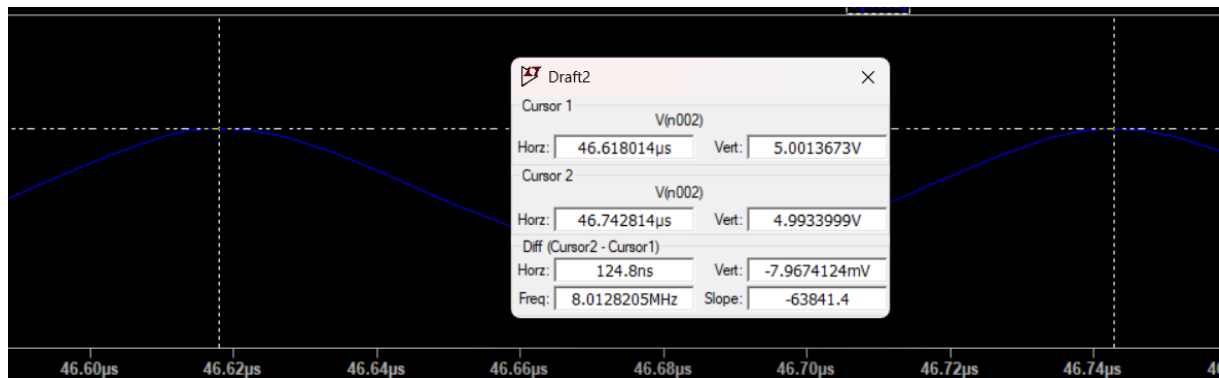


Fig. 17: Frequency of the diode voltage

The reverse bias capacitance can be found from the resonant frequency formula given below.

$$f = \frac{1}{2\pi\sqrt{LC}}$$

From there with  $L=10\mu H$  and  $f=8.01Mhz$ ,  $C$  value is calculated as 39.5pF.



- j) Including the  $0.4\Omega$  series resistance of the inductor in continuous case, figures below show the output and input power graphs respectively.

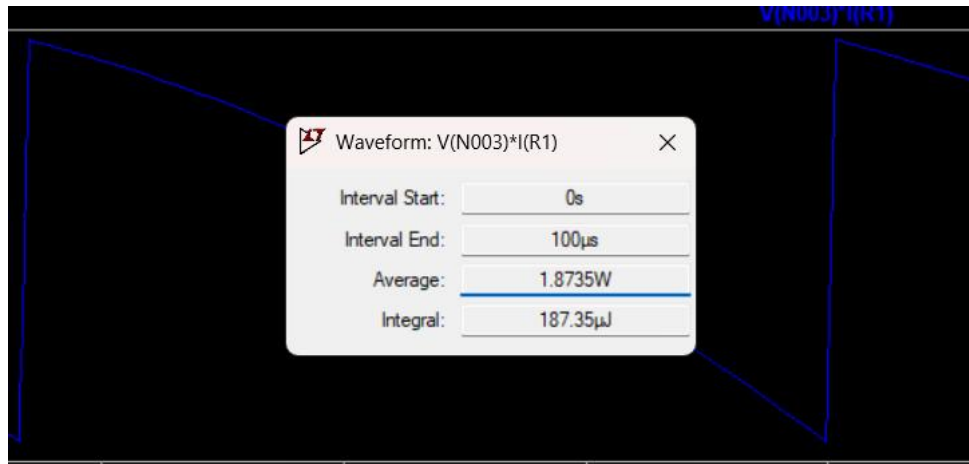


Fig. 18: Output power

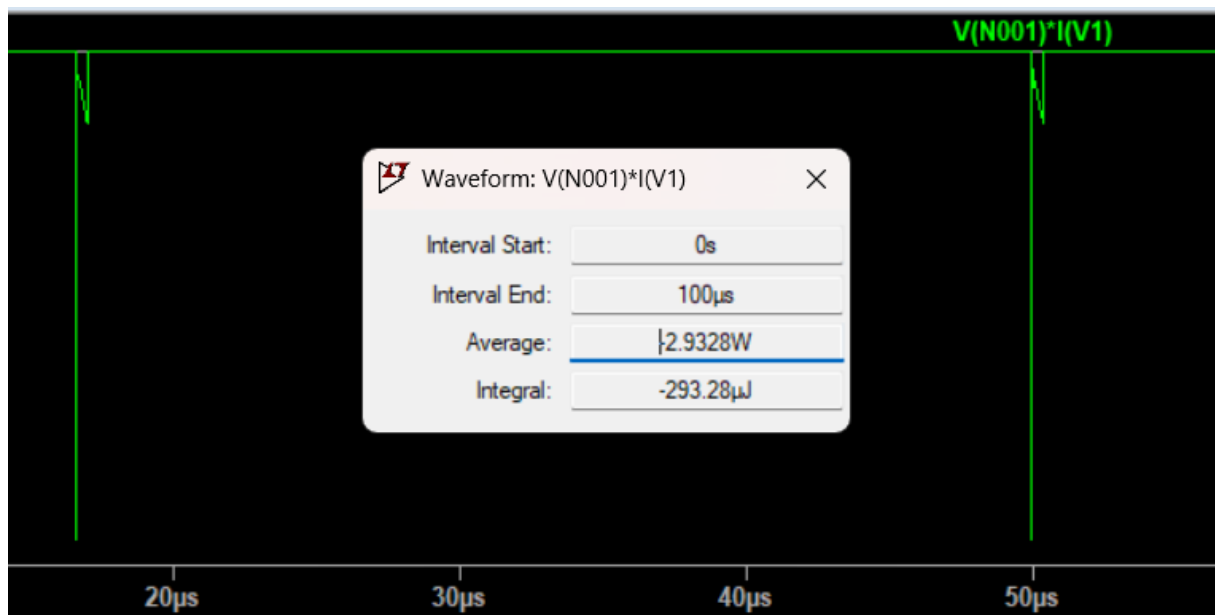


Fig. 19: Input power

$$\eta = \frac{P_{out}}{P_{in}} * 100$$

Using the above equation, the efficiency of the converter is calculated as 63.8%.