



EEE 102 Term Project: Parking Lot Barrier System

Orkun İbrahim K  k

22003656

EEE102 – 01

Youtube video link:

<https://youtu.be/tkgmV18fxQw>

Purpose

The aim of this project is implementing the barrier system in parking lots to basys 3 FPGA by using some other external components

Design Specifications

The design has 3 inputs and 1 output. 2 of the 3 inputs are “clock” and “clear” inputs which are present in all designs. The other input is “duty_cycle”, which is related to signals from infrared sensor. “Pwm” (pulse-width modulation) is the output of the circuit which drives the servo motor reagarding the signals coming from the infrared sensor.

Methodology

My design takes signals from the infrared sensor and transfers these signals to basys 3 and via the code that I have written, servo motor starts working. I used a 5V adapter in order to give power to my servo motor because basys 3 can only provides 3,3V which is not enough for servo motor to work. I used a 12V 2A adapter cable for my adapter. I used a logic level converter to connect the servo motor to basys 3 FPGA. I connected my infrared sensor directly to basys 3 FPGA. I used JA and JC pins on my basys 3 FPGA to program the infrared sensor and servo motor via VHDL.

 


Figure 1.a: Breadboard design

 


Figure 1.b: Complete design

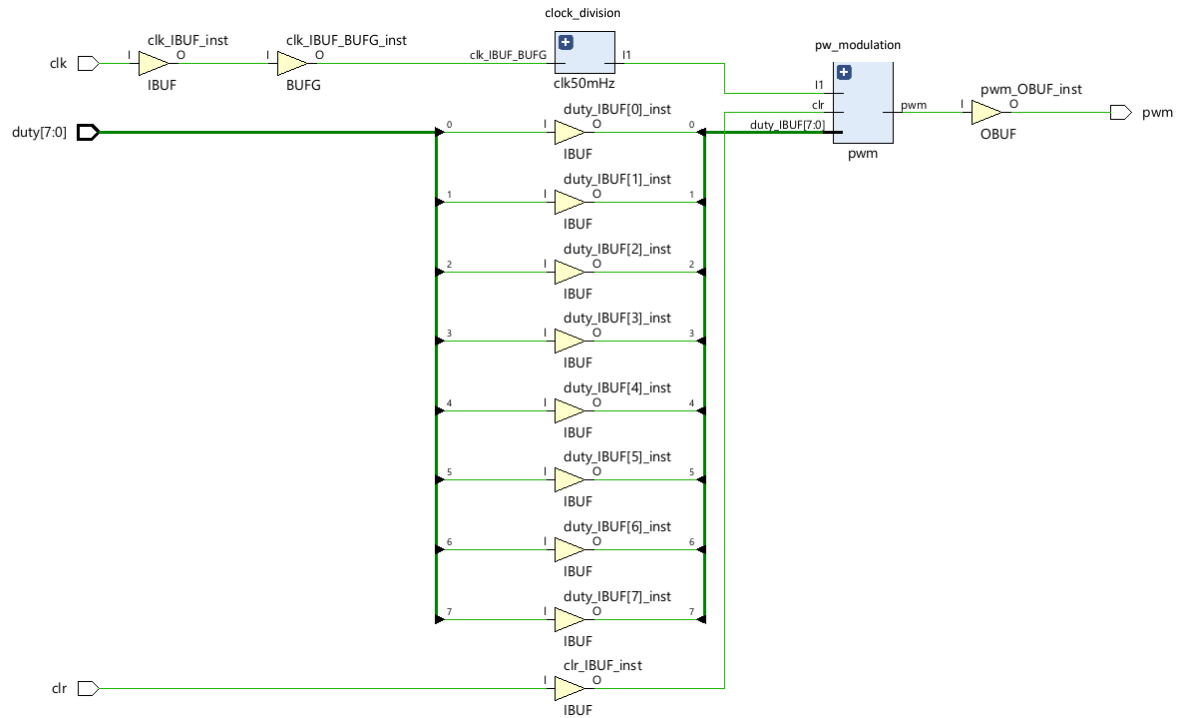


Figure 2: Schematic

VHDL Code

main_module.vhd

```
library IEEE;

use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_unsigned.all;

entity main_module is
    port(
        clear : in std_logic;
        clock : in std_logic;
        duty_cycle : in std_logic_vector (7 downto 0);
        pw_modulation : out std_logic
    );
end main_module;

architecture main of main_module is
```

```

signal n_clk : std_logic;

begin

clock_division: entity work.clk_freq

    port map(

        clock => clock, reset => '0', clock_output => n_clk);

Pulse_width: entity work.pw_modulation

    port map(

        clear => clear, clock => n_clk, duty_cycle => duty_cycle, period => "11001000",
        pw_modulation => pw_modulation);

end main;

```

[clk_freq.vhd](#)

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

```

```

entity clk_freq is

```

```

    Port (

        clock   : in  STD_LOGIC;

        reset   : in  STD_LOGIC;

        clock_output: out STD_LOGIC

    );

```

```

end clk_freq;

```

```

architecture freq of clk_freq is

```

```

    signal temp: STD_LOGIC;

    signal s_count : integer range 0 to 5000 := 0;

```

```

begin

```

```

    clock_division: process (reset, clock) begin

        if (reset = '1') then

```

```

    temp <= '0';
    s_count <= 0;
elseif rising_edge(clk) then
    if (s_count = 5000) then
        temp <= NOT(temp);
        s_count <= 0;
    else
        s_count <= s_count + 1;
    end if;
end if;
end process;

clock_output <= temp;
end freq;

```

[pulse_width.vhd](#)

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_unsigned.all;
entity pulse_width is
    port(
        clear : in std_logic;
        clock : in std_logic;
        duty_cycle : in std_logic_vector (7 downto 0);
        period : in std_logic_vector (7 downto 0);
        pw_modulation : out std_logic
    );
end pw_modulation;

architecture behavioral of pw_modulation is
    signal s_count : std_logic_vector(7 downto 0);

```

```

begin
    proc_count: process(clock, clear)
    begin
        if clear = '1' then
            s_count <= "00000000";
        elsif clk event and clk = '1' then
            if s_count = period -1 then
                s_count <= "00000000";
            else
                s_count <= s_count +1;
            end if;
        end if;
    end process proc_count;
    pwm_output: process(s_count, duty_cycle)
    begin
        if s_count < duty_cycle then
            pw_modulation <= '1';
        else
            pw_modulation <= '0';
        end if;
    end process pwm_output;
end behavioral;

```