

EEE412 “High Gain Amplifier” Project Report

Introduction

In this report, the design steps of a “High Gain Amplifier (HGA)” using a single BFU520W BJT will be shown. The center frequency of the HGA is assigned to be $f = 0.39\text{GHz}$. The design specifications are listed below:

- Source and load resistances are both 50Ω
- Unconditionally stable at all frequencies (40MHz to 2GHz)
- Bandwidth: 10%
- Input return loss > 12dB in the band
- Output return loss > 12dB in the band
- Gain > $19 - 6.5 \times f$ (GHz) dB (f is the center frequency)
- Gain variation $\leq \pm 0.5\text{dB}$ in the band

Additionally, the PCB layout of the circuit schematic will be created with available components.

Methodology

The previously designed circuit schematic has a high-pass input matching network in the input side, therefore, it is changed to a low-pass topology. The new version of the circuit schematic is given in the figure below.

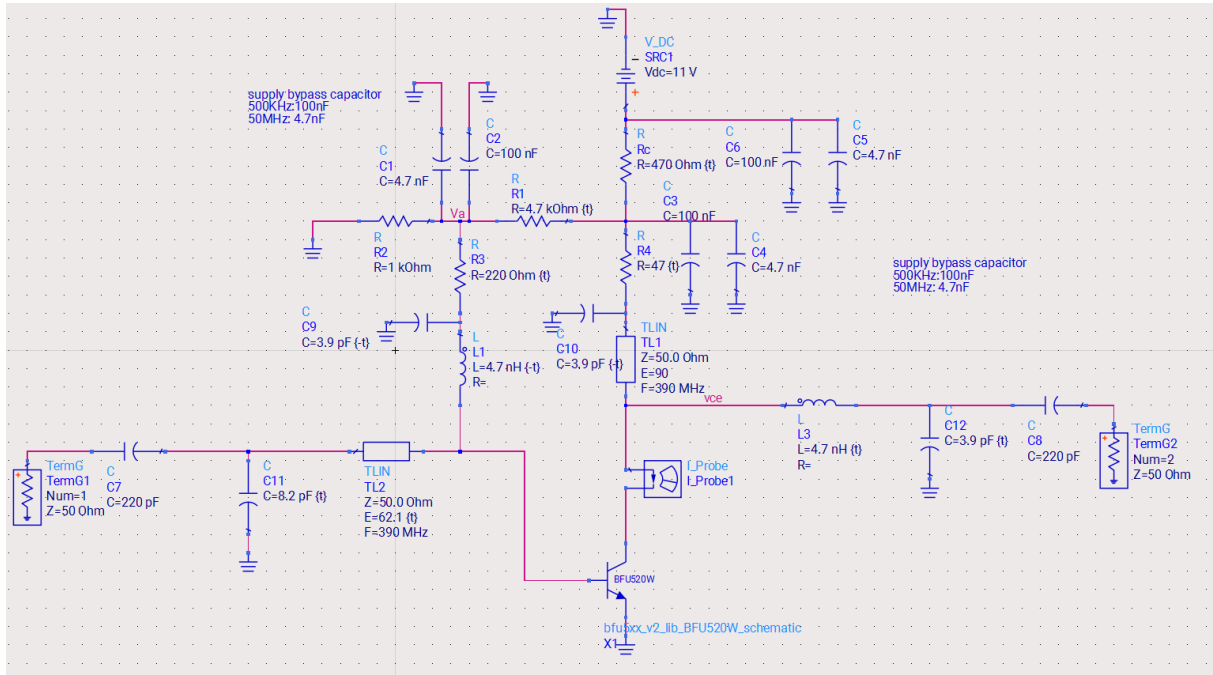


Fig. 1: Revised circuit schematic with available components used

Now, to be able to create a correct layout, lumped elements and transmission lines are changed so that their W and L values determined. Fig. 2 is the final value of the circuit schematic for the analysis purposes.

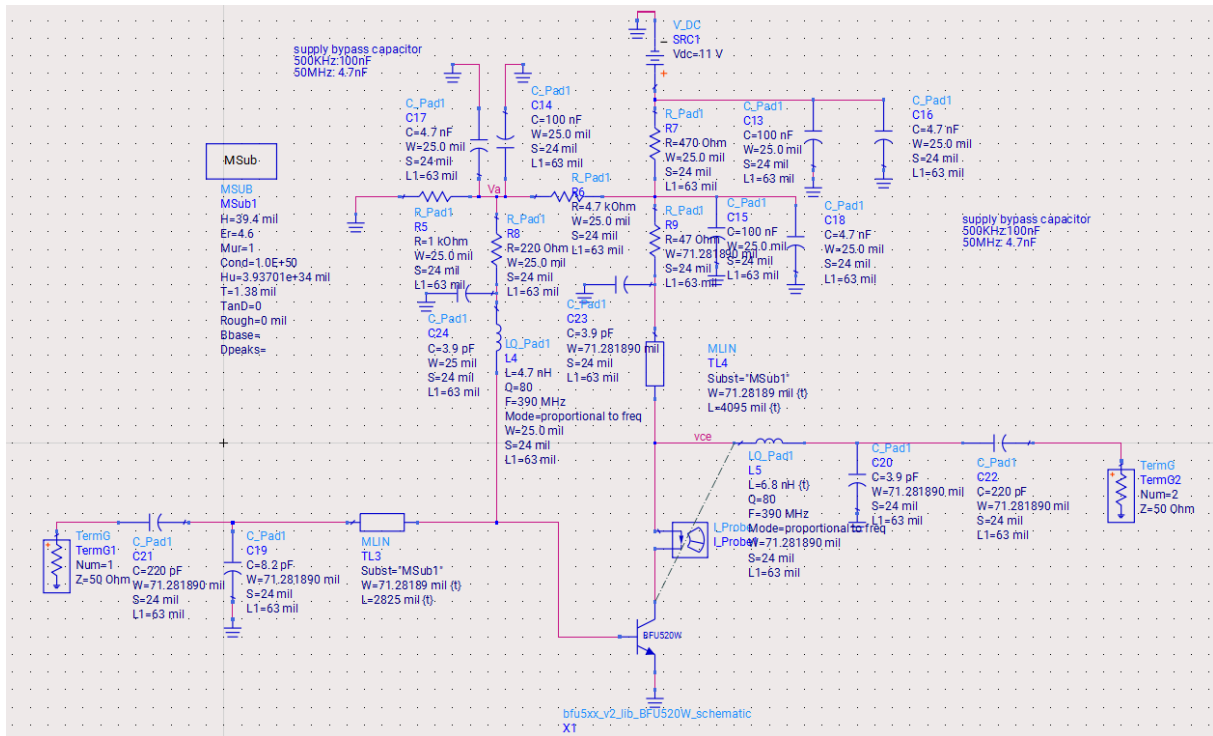


Fig. 2: Simulation circuit schematic

Analysis

Initially, the biasing of the circuit will be checked. The operation points of the transistor are chosen as $V_{CE}=5V$ and $I_C=10mA$. Fig.3 shows the measured V_{CE} voltage from the schematic.

 


Fig. 3: V_{CE} voltage

Fig. 4 shows the collector current I_C of the transistor.

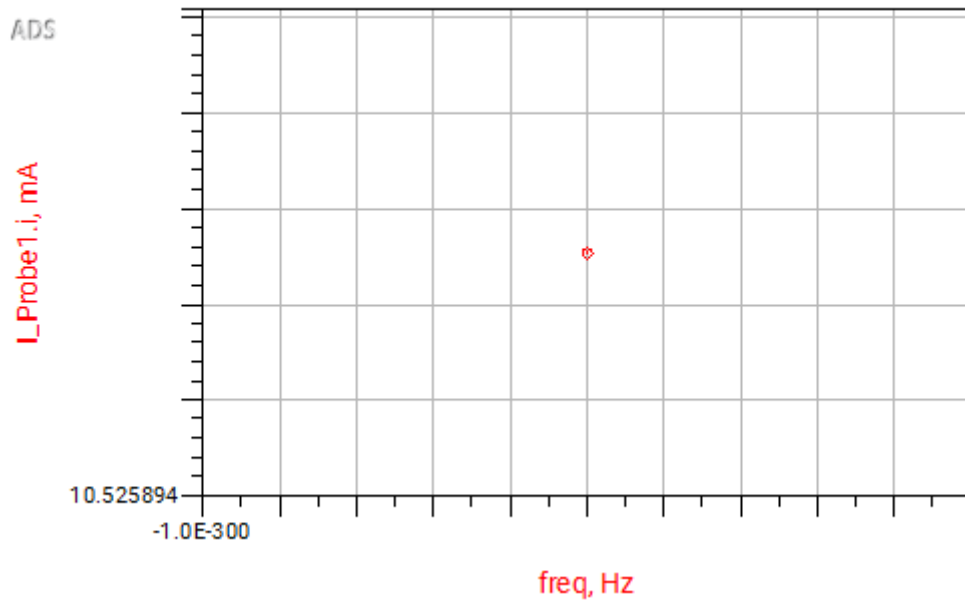


Fig. 4: I_C of the transistor

As mentioned, the chosen operating point is $V_{CE} = 5V$ and $I_C = 10mA$. From Fig. 3 and Fig. 4, it can be seen that a V_{CE} of 5.08V is achieved and an I_C of 10.5mA current is achieved. The biasing of the circuit is done successfully. Additionally, the current going through R_2 resistor is set to $10I_B$, which is 1.053mA calculated earlier. Fig. 5 shows the measured voltage value at that node. R_2 value is chosen as 1K Ω .

 


Fig. 5: Voltage at node A (V_0)

Using the Ohm's Law, the current going through R_2 resistor can be calculated.

$$V = IR$$

$$I = \frac{V}{R} = \frac{0.878}{1000} = 0.878mA$$

This value is calculated as 1.053mA initially, and at the simulation, a current value of 0.878mA is achieved. This concludes that the biasing network of the circuit is satisfactory.

To determine whether the circuit is stable, stability factor (K) of the circuit is plotted. If $K > 1$, circuit is stable. Fig. 6 shows the stability factor plot of the circuit by indicating the minimum point.

 


Fig. 6: Stability factor plot of the circuit

S_{11} and S_{22} plots of the circuit are given in the figures below respectively for the whole frequency range (40MHz – 2GHz).

 


Fig. 7: S_{11} plot of the circuit

 


Fig. 8: S_{22} plot of the circuit

And for the 10% bandwidth frequency range (370.5MHz – 409.5MHz), the S_{11} and S_{22} plots are given below respectively.

 


Fig. 9: S_{11} plot of the circuit inside the band

As seen from Fig. 9, at the center frequency 390MHz, S_{11} is measured as -22.164dB. Inside the band, the maximum value measured is -15.199dB, which is lower than the requirement -12dB. This requirement is also satisfied.

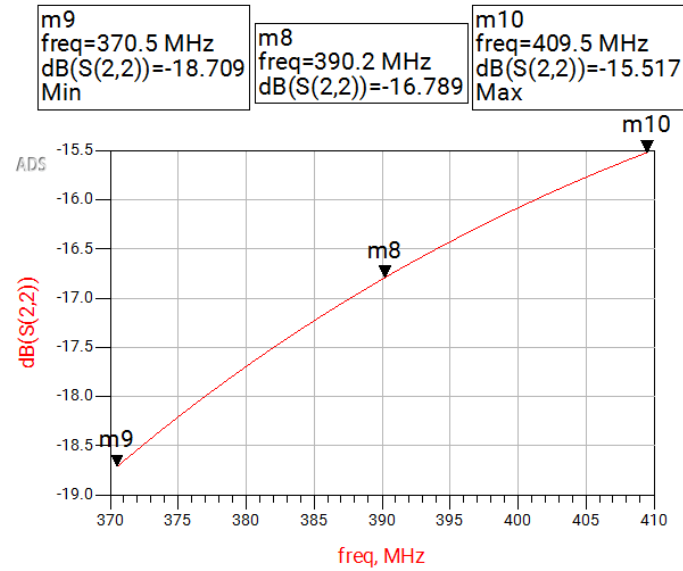


Fig. 10: S_{22} plot of the circuit inside the band

As seen from Fig. 10, at the center frequency 390MHz, S_{22} is measured as -16.789dB. Inside the band, the maximum value measured is -15.517dB, which is lower than the requirement -12dB. This requirement is also satisfied.

The S_{21} plot of the circuit is given in Fig. 11. The threshold gain is determined from the equation given in the Introduction. It was calculated as 16.465dB.

 


Fig. 11: S_{21} plot of the designed HGA

The minimum gain achieved inside the band is measured as 17.371dB, which is above the threshold value, 16.465dB. The gain requirement also satisfied. Moreover, the maximum gain achieved inside the band is measured as 17.492dB. The gain variation in the band is measured as 0.121dB, which is less than 0.5dB as specified in the design specifications. This requirement is also satisfied.

The noise figure of the circuit inside the band is shown in Fig. 12.

 


Fig. 12: Noise figure of the circuit inside the band

As seen from Fig. 12, at the center frequency, the measured noise figure of the HGA is 2.02, and inside the band, the highest noise figure value is measured as 2.206.

This concludes the analysis of the HGA with a full satisfaction of the design specifications.

The next task is to make necessary changes in the length of transmission lines so that they will fit inside the determine PCB dimensions.

PCB design

Firstly, I swapped the ground connections to VIAGND connections. For the emitter-ground connection, I used two parallel VIAGND's because each VIAGND acts like a small inductance, connecting them in parallel reduces the inductance by half, which reduces the effect on dB gain of the circuit. For each shunt capacitor, I used one VIAGND per shunt capacitor. Total number of VIAGNDs used in the schematic is 14 in total. Furthermore, VIAGND's changed the S_{11} , S_{22} , and Gain of the circuit. Therefore, an additional tuning performed on the schematic to get the desired results again.

At the both end of the matching networks, a 50Ω transmission line is inserted until reaching the side of the PCB. These are for the SMA connector. For the specified values, at 390MHz, a 50Ω transmission line has a measured width(W) of 71.28189mils.

To fit the design into 2300x1000 mils board, I changed the length of the used transmission lines in the circuit, and bended them to use the area effectively. In Fig. 2, TL3 has a total length of 2825mils. With tuning, the new length of that transmission line determined as 2250mils. Again from Fig. 2, TL4 has a total length of 4095mils. With tuning, the new length of that transmission line determined as

3059mils. Fig. 13 shows the source and load unit stability circles and Fig. 14 shows the plot for stability factor (K) from 40MHz to 2GHz.

 


Fig. 13: Source and load unit stability circles

 


Fig. 14: Stability factor (K) plot

As seen from Fig. 13, the stability circles are outside the unity Smith chart, and looking at Fig. 14, stability factor (K) value is always above 1. Those results show that circuit is unconditionally stable at all frequencies from 40MHz to 2GHz.

The S_{11} and S_{22} plots in dB inside the 10% bandwidth are given in below figures respectively.

 


Fig. 15: S_{11} plot of the final schematic

As seen from the above figure, inside the band, the maximum value is measured as -16.891, which is less than -12dB, as specified in the design specifications.

 


Fig. 16: S_{22} plot of the final schematic

As seen from the above figure, inside the band, the maximum value is measured as -14.318, which is less than -12dB, as specified in the design specifications.

The dB gain of the circuit is given in Fig. 17.

 


Fig. 17: Gain of the final version of the circuit

Inside the band, the maximum gain is measured as 17.497dB and minimum gain is measured as 17.365dB. The gain variation inside the band is calculated as 0.412dB, which is less than 0.5dB. Additionally, at the center frequency, the dB gain is measured as 17.365dB.

Finally, the noise figure of the circuit inside the band is depicted in the below figure.


 


Fig. 18: Noise figure of the final version of the circuit

The highest noise figure inside the band is measured at 409.5MHz with a value of 2.605.

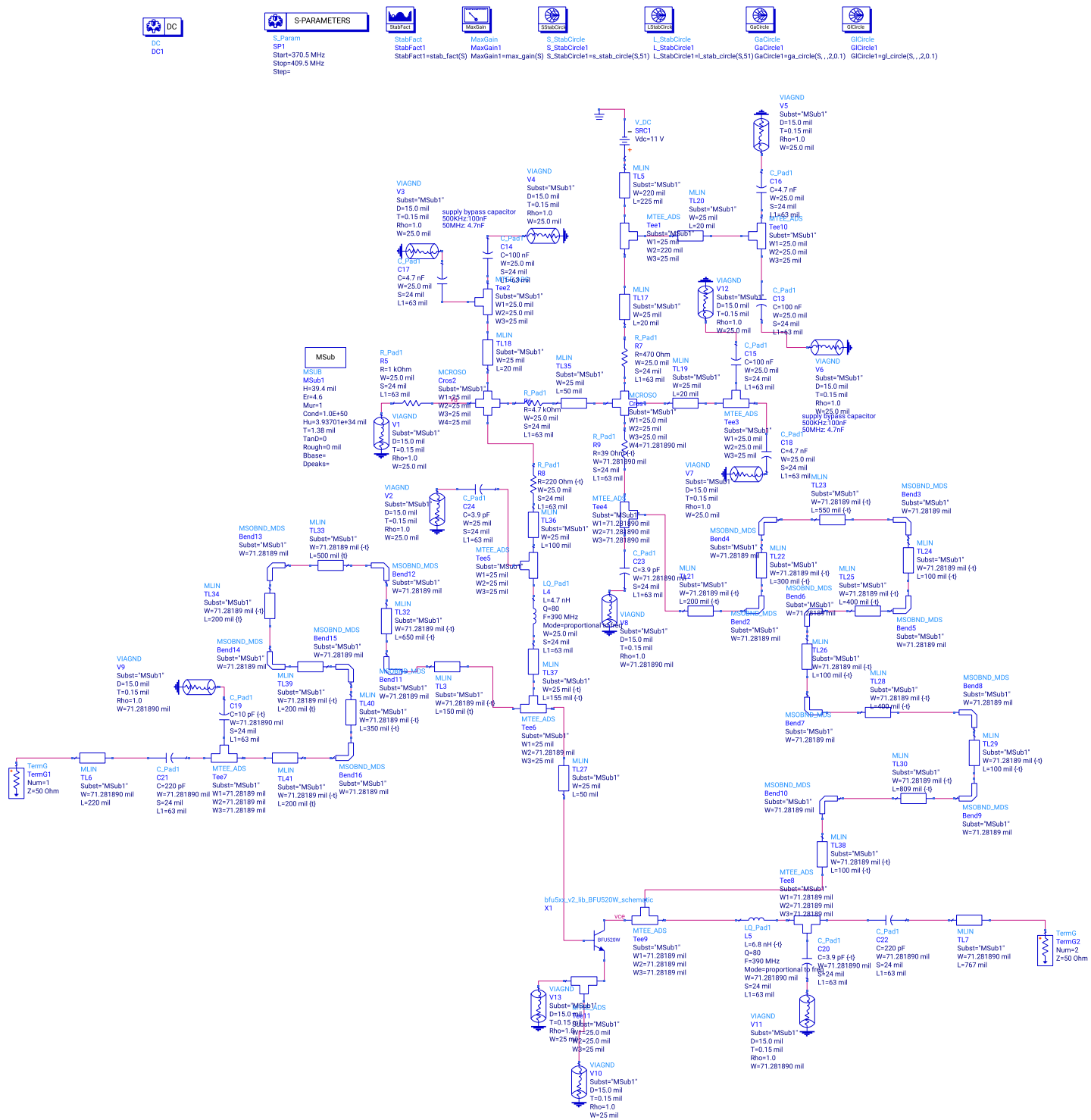The schematic of the circuit is given in the following page.



The board outline is specified as 2300x1000mils. Converting to mm, it is 58.4x25.4 mm. Fig. 19 shows the ruler depicting the sides of the board.

 


Fig. 19: Board outline measurements

The top layer image of the designed PCB is given in Fig. 20.

 


Fig. 20: Top layer of the designed PCB

The drill locations are also given in the following figure.

 


Fig. 21: Drill locations of the designed PCB

In the following page, the designed layout of the circuit can be seen. As mentioned, for the SMA connectors, a transmission line of 50Ω is added and extended to the sides of the board.

