

## EEE419 Lab 1 Preliminary

### Analysis:

- a) When only the NE555 circuit is on the breadboard with the BC308 pnp transistor and applied  $V_d$  from the power supply (12V), waveform at the node  $V_p$  can be seen in Fig. 1. The voltage varies between  $-V_d$  (-12V) and -200mV. The specifications says it should vary between  $-V_d$  and zero.

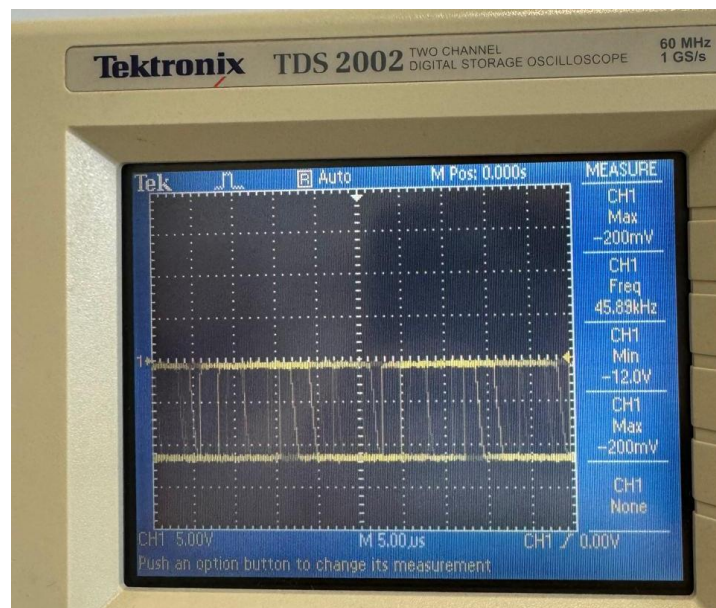


Fig. 1: Voltage at  $V_p$

- b) Now, the whole board is set up on the breadboard. For this question  $R_L=560\Omega$ . Fig. 2 shows the voltage waveform at node  $V_x$  from the LTspice simulation. Fig. 3 shows the voltage at  $V_x$  measured on oscilloscope. The waveforms resemble to each other. Also,  $V_x$  varies between -13V to 800mV. Per the specification indicates, the voltage should vary between  $-V_d$  (-12V) and 0.6V. The values are near with a slight error included.

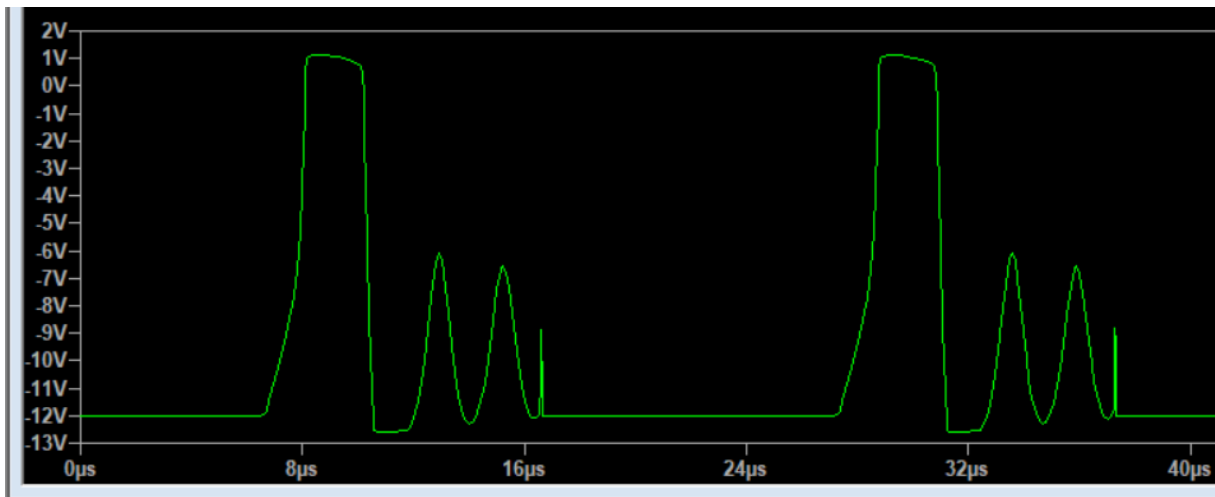


Fig. 2: Voltage at  $V_x$

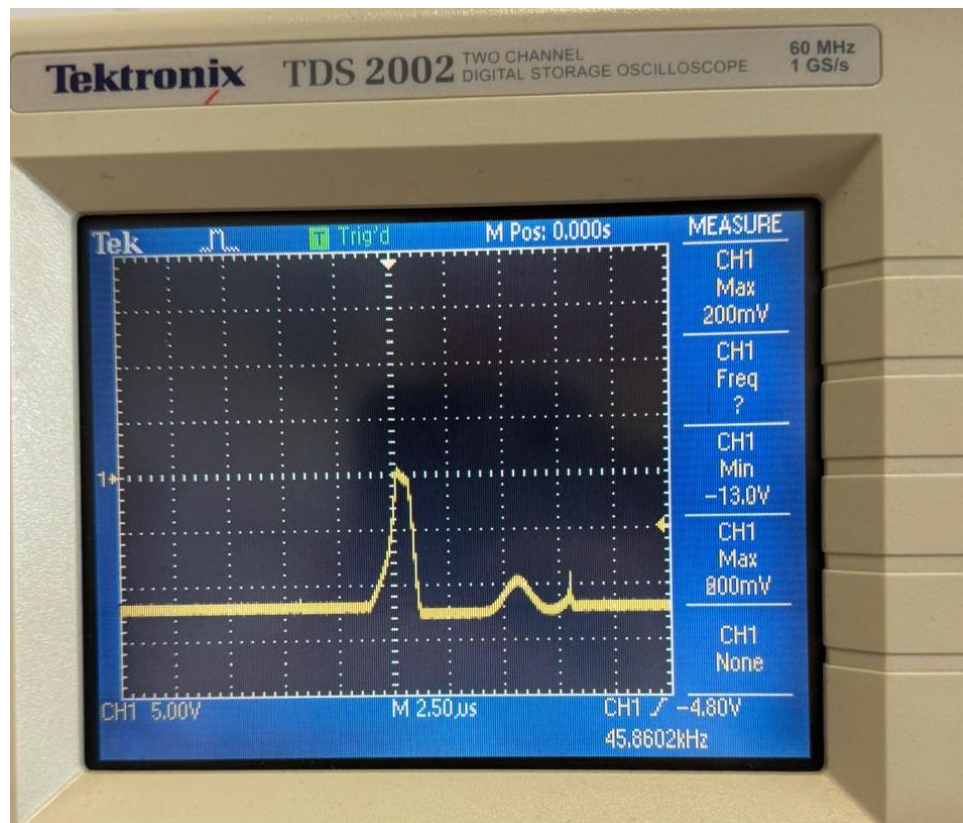


Fig. 3: Voltage at  $V_x$  measured from oscilloscope

c) The  $R_{L1}$  value is changed to  $10\Omega$  and asked values are recorded (Table 1).

Table 1:  $R_L=10\Omega$  measurements

	$V_d$	$I_d$	$R_L = R_{L1}$	D	$V_o$	$\eta(\%)$	$V_{ripple}$
Preliminary	12V	355mA	$10\Omega$	0.458	5.5V	72%	52mV
Experimental	12V	388mA	$10\Omega$	0.418	0.551	66%	100mV

Fig. 4 shows the  $V_d$  and  $I_d$ . Fig. 5 shows the  $T_s=22\mu s$  and Fig. 6 shows the  $t_{on}=9.2\mu s$  waveforms (Inductor current waveforms). The waveform is a bit distorted because of the breadboard's insensitivity. When I connected the GND of the oscilloscope probe near the load resistor, the waveform changed and be as expected, a triangle. D is calculated as 0.418. The efficiency is calculated as 66% in the experiment, where it is measured as 72% in the simulation. The difference may caused by the inductor windings and its series resistance, breadboard's insensitiveness. The output voltage ripple  $V_{ripple}$  is measured as 100mV (Fig. 7). However, as Prof. Atalar said, 100mV is a reasonable value for output voltage ripple. Therefore, with a slight error included, all of the value measured and calculated in the experiment are near to values measured and calculated in the LTspice simulation.

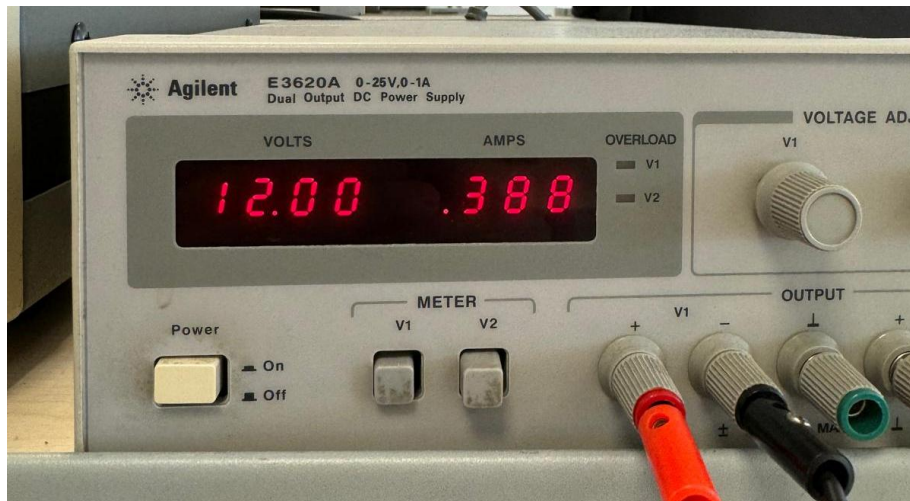


Fig. 4: Input voltage and current

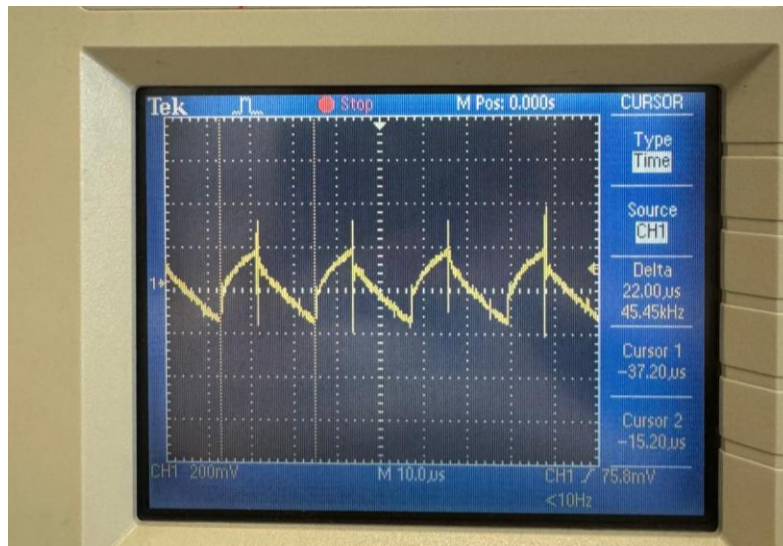


Fig. 5:  $T_s$  value from inductor current

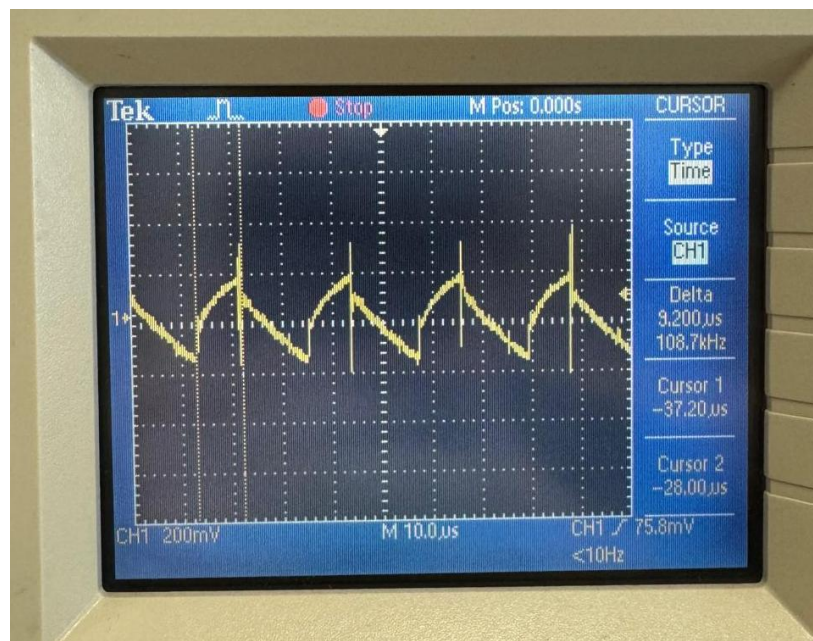


Fig. 6:  $t_{ON}$  value from inductor current





Fig. 7: Output voltage ripple  $V_{ripple}$

d)  $V_x(t)$  is the diode voltage. Fig. 8 shows the  $V_x$  voltage in LTspice and Fig. 9 shows the  $V_x$  voltage measured from oscilloscope.


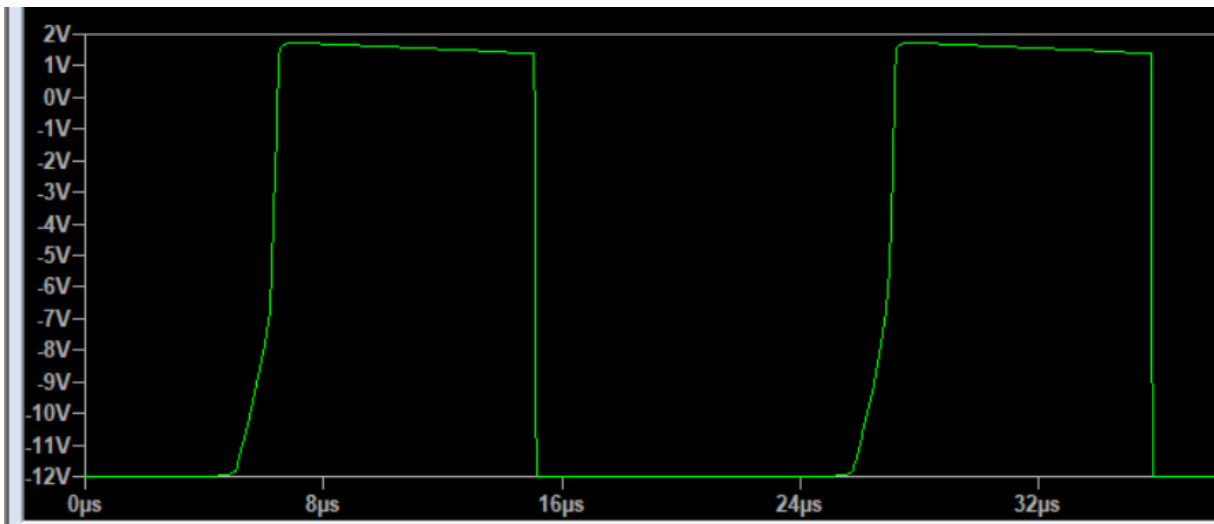


Fig. 8:  $V_x$  voltage

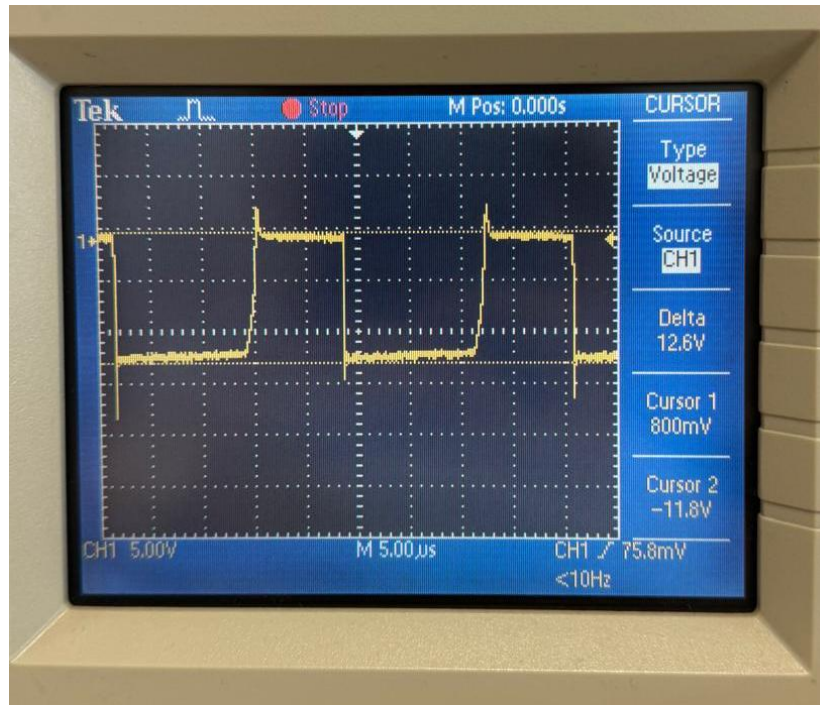

*Fig. 9: Voltage  $V_x$  measured from oscilloscope*

In the simulation,  $V_x$  varies between  $-V_d$  (-12V) to 1.7V. In the experiment, voltage varies between -11.8V and 800mV. The waveforms are exactly the same.

For  $i_D(t)$ , I measured  $v_R(t)$  and multiplied it with 2 because of the two parallel connected  $1\Omega$  resistors. Fig. 10 shows the  $i_D(t)$  measured from LTspice and Fig. 11 shows the  $v_R(t)$  waveform measured from oscilloscope. The result will be multiplied by 2.

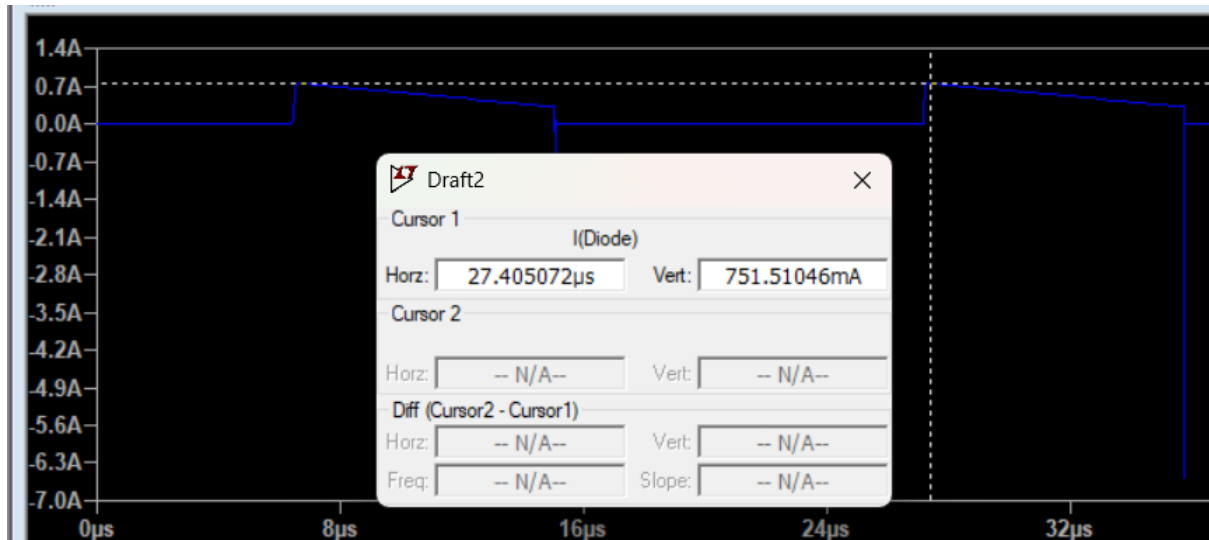


Fig. 10:  $i_D(t)$  diode current waveform

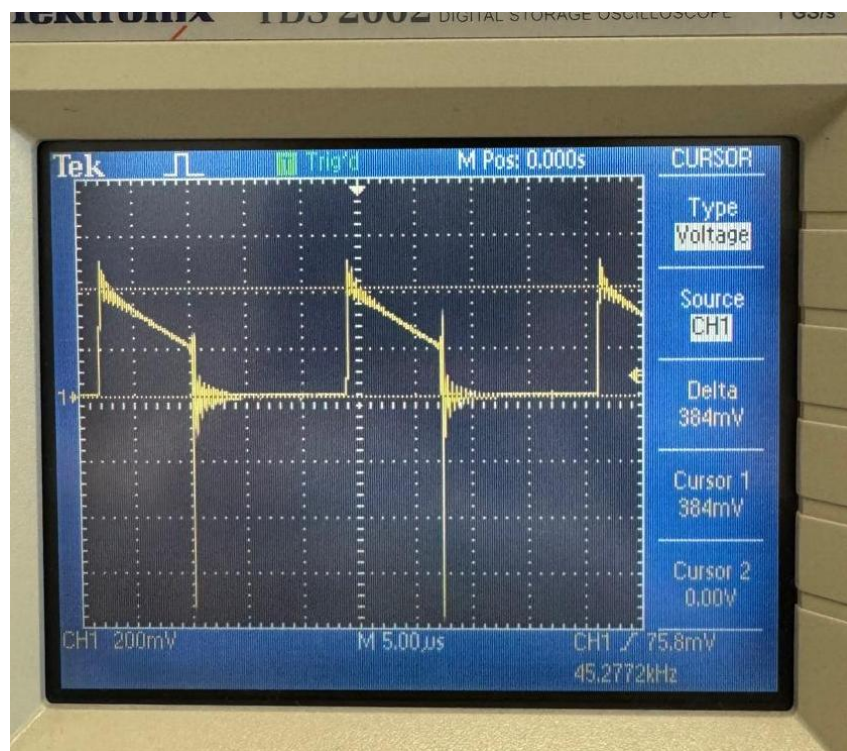


Fig. 11: Diode voltage  $v_R(t)$  measured from oscilloscope

As seen from Fig. 11, the peak value is 384, multiplying by 2 gives 768mA. Whereas in the simulation, max diode current value is 751mA. The values are exactly the same as expected.

- e) Now, the load resistance  $R_{L2}=47\Omega$ . In order to get the desired output voltage  $V_o=5.5V$ , I swapped the resistors  $R_A$  and  $R_B$ . By changing their values, the desired output voltage is achieved (Fig. 12).

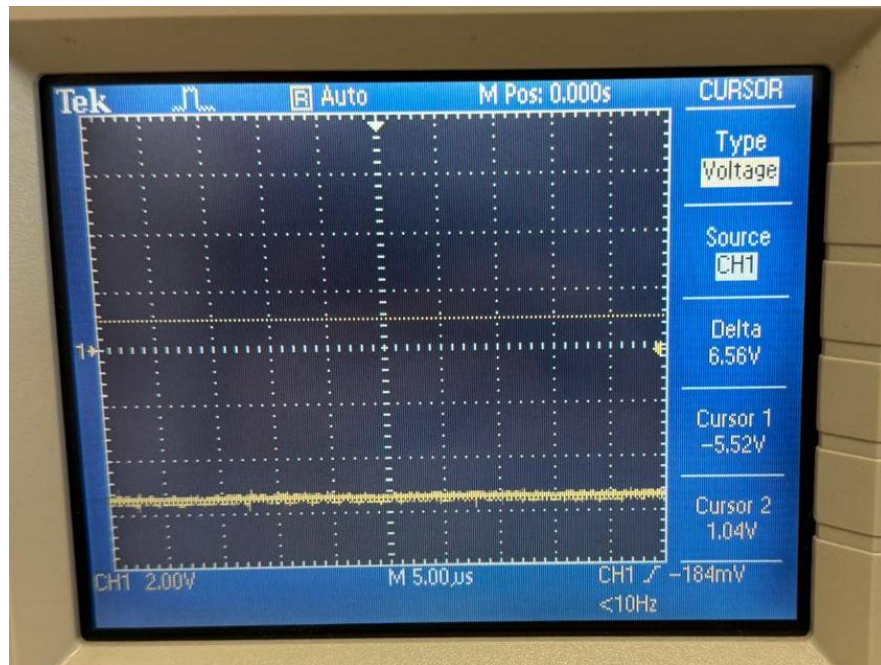


Fig. 12: Output voltage when  $R_{L2}=47\Omega$

Table 2:  $R_L=47$  measurements

	$V_d$	$R_{L2}=R_L$	D	$V_o$
Preliminary	12V	$47\Omega$	0.462	5.5V
Experimental	12V	$47\Omega$	0.488	5.52V

In LTspice simulation, the duty cycle is measured as 0.462 from the inductor current graph. In the experiment, Fig. 13 and Fig. 14 shows the  $T_s$  and  $t_{ON}$  values respectively.



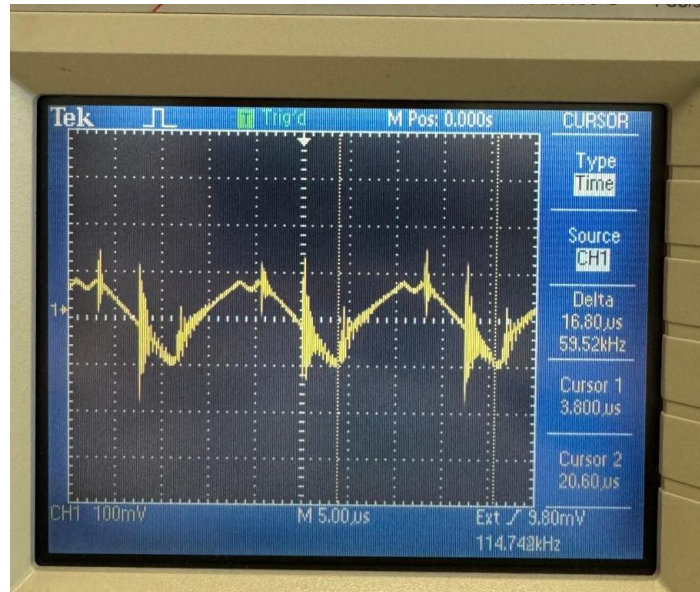


Fig. 13:  $T_s$  when  $R_L=47\Omega$

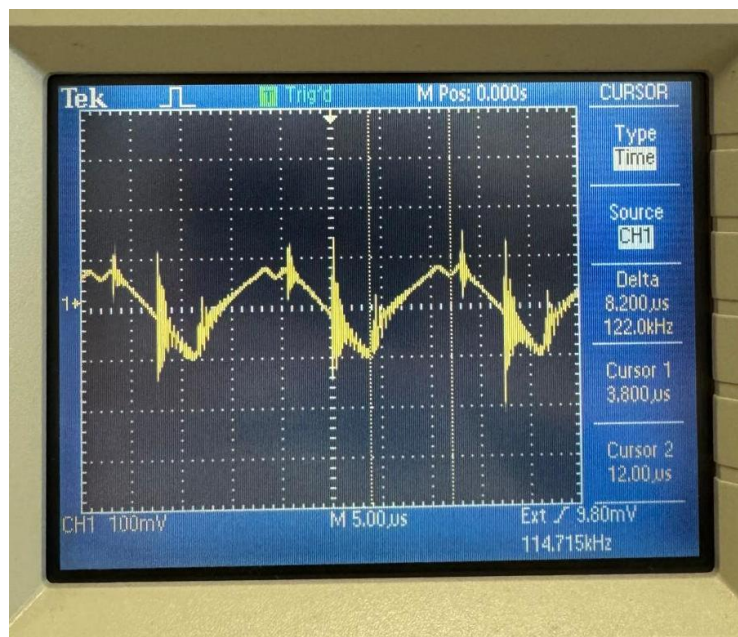


Fig. 14:  $t_{ON}$  value when  $R_L=47\Omega$

$T_s$  value is measured as  $16.8\mu s$  and  $t_{ON}$  value is measured as  $8.2\mu s$ . Whereas in the LTspice simulation,  $T_s=16.36\mu s$  and  $t_{ON}=7.54\mu s$ . The values are near to each other. As stated in Table 2,  $D=0.462$  for simulation and  $D=0.488$  for experiment. The values are reasonable.