

$$V_- = \left(\frac{R_1}{R_1 + R_2} \right) V_{out}$$

$$\left(\frac{V_{out}}{V_+} = ? \right)$$

$$0 = \frac{V_{out} - \left(\frac{R_1}{R_1 + R_2} \right) V_{out}}{R_2} + \frac{V_{out} - A(V_+ - \frac{R_1}{R_1 + R_2} V_{out})}{R_{out}}$$

Let $\frac{R_1}{R_1 + R_2} = \beta$ then,

$$V_{out} (R_{out} - \beta R_{out}) = V_{out} (R_2 + \beta R_2) - A V_+ R_2$$

$$V_{out} [(1 - \beta) R_{out} - (1 + \beta) R_2] = - (A \cdot R_2) V_+$$

$$\frac{V_{out}}{V_+} = \frac{A \cdot R_2}{(1 + \beta) R_2 + (1 - \beta) R_{out}} \quad \text{if } R_{out} = 0 \quad \frac{A}{1 - \beta} = \boxed{\frac{A}{1 + A \cdot \frac{R_1}{R_1 + R_2}}} \quad \checkmark \text{ holds}$$

$$\frac{V_{out}}{V_+} = \frac{A R_2}{\left(1 + A \cdot \frac{R_1}{R_1 + R_2} \right) R_2 - \left(1 - \frac{R_1}{R_1 + R_2} \right) R_{out}}$$

b) $A_v = \frac{A}{1 - A \cdot \frac{R_1}{R_1 + R_2}}$, if $A = 1000001$ this equation becomes as follows:

$$A_v = \frac{A}{A \cdot \frac{R_1}{R_1 + R_2}} = \boxed{\frac{R_1 + R_2}{R_1} = 5}$$

c) with R_{out}


$$A_v = \frac{100000 \cdot 1k}{\left(1 + 100000 \cdot \frac{1}{5} \right) 4k - \left(1 - \frac{1}{5} \right) 100k} = \boxed{1.38}$$

without R_{out}

$$\boxed{A_v \approx 5}$$

so without R_{out} , OPAMP gain is large compared to with R_{out} case. the feedback wants to correct this value but OPAMP couldn't. However, as seen in the without R_{out} case, due to feedback we get 5 gain.

$$\frac{1}{4} \left[2A^2 + 2A^2 + 4A^2 \right] \quad \text{for } 2A^2 = 10^5$$
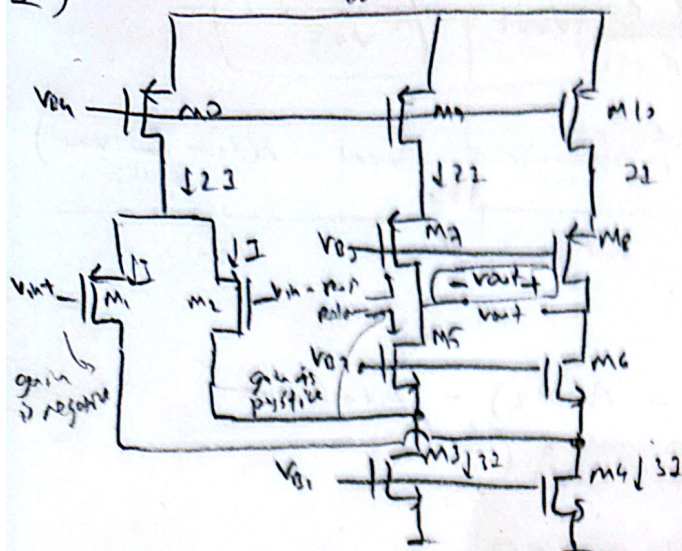
$$V_{DD} = 3.3V$$


$$\left(\frac{w}{L}\right)_{1,2} = 2 \left(\frac{w}{L}\right)_{5,6}$$

$$\mu_{\text{Co}} = \mu_{\text{Fe}} \cos \gamma \approx 0$$

$$\lambda_n = \lambda_p \quad r_{05} = r_0 \quad g_{m5} = g_m$$

$$\left(\frac{W}{L}\right)_S = \left(\frac{W}{L}\right)_D = \frac{10 \mu\text{m}}{1 \mu\text{m}}$$

a) - rout +

$$b) \frac{1}{2} \mu_e \cos\left(\frac{W}{L}\right) (V_{G1} - V_{th})^2 = 22$$

$$\frac{1}{2} \frac{\mu_p C_{ox}}{\mu_n C_{ox}} \left(\frac{W}{L} \right)_{T,e} (V_{G1} - V_{th})^2 = 22$$

$$\Rightarrow \left(\frac{w}{L}\right)_{7,8} = 4 \left(\frac{w}{L}\right)_{5,6} = \left(\frac{w}{L}\right)_{9,10} = \left(\frac{w}{L}\right)_0$$

$$\frac{1}{2} m \cos\left(\frac{\omega}{L}\right)_{\text{L.H.}} (V_{G1} - V_{th})^2 = 37$$

$$\left(\frac{W}{L}\right)_{3,4} = \frac{3}{2} \left(\frac{W}{L}\right)_{5,6}$$

(c) $A_v = -G_m R_{out}$

$$G_M = -g_{M1} = -g_M$$

Route RUP // edon (gross)

$$R_{\text{up}} = g_m r_{o2} r_{o9} = g_m r_o^2$$

$$R_{\text{down}} = \frac{g_m \sin \theta}{g_m \sin \theta} \left(\frac{r_{02} // r_{01}}{\frac{10}{2}} \right) = \frac{g_m r_o^2}{2}$$

$$P_{\text{out}} = \frac{gmro^2 - \frac{gmro^2}{2}}{\frac{2gmro^2}{2} + \frac{gmro^2}{2}} = \frac{1}{3} gmro^2 \Rightarrow A_v = -\frac{(gmro)^2}{3}$$

2) Total noise contributors: M_1 , M_9 , and M_3 . Due to source degeneration, noise is not amplified, so that I can ignore the contribution coming from the transistors M_0 , M_7 , and M_5 . Same goes for the other branch of course.

$$\frac{m_1}{4hT \delta g m_1} = \frac{1}{4hT \delta g}$$

mg current to voltage
conversion

$4kT \times gm_9 \cdot R_{out}^2$ $4kT \times gm_9$

$gm_1^2 \cdot R_{out}^2$ gm_1^2

gain of the
opamp

$$\frac{m_2}{4hT_0 g m_2}$$

Total via

$$2 \times 4 kT \delta \left[\frac{1}{g_{m1}} + \frac{g_{m2}}{g_{m1}^2} + \frac{g_{m3}}{g_{m1}^2} \right]$$

$$d) V_{out,max} = V_{in,max} = V_{DD} - 2V_{ov}$$

$$V_{out} = V_{in} = V_{OV} + V_{th}$$

3) $\Delta V_{BE} = V_T \ln(n)$

node of the opamp = $V_y - V_x$

$V_{EB} = V_T \ln\left(\frac{I_c}{I_1}\right)$ normally

$V_{EB1} - V_{EB2} = V_T \ln(n)$ what we want

$\begin{matrix} \uparrow & \uparrow \\ A_{2s} & B_{2s} \end{matrix} \Rightarrow V_T \ln\left(\frac{I_c}{A_{2s}}\right) - V_T \ln\left(\frac{I_c}{B_{2s}}\right) = V_T \left[\ln I_c - \ln A_{2s} - \ln I_c + \ln B_{2s} \right]$

a) $A_2 = nA$, $A_1 = A$ $\Rightarrow V_T \ln\left(\frac{B_{2s}}{A_{2s}}\right)$

b) $\beta_n = \frac{R_{down}}{R_{down} + R_{up}}$ $\begin{matrix} \text{BJT} \\ \downarrow \\ \frac{1/g_{m1} \parallel R_o}{1/g_{m1} \parallel R_o + r_{o1}} \end{matrix}$

$\begin{matrix} B = n \\ A = 1 \end{matrix}$

$\beta_p = \frac{(1/g_{m2} + R_1) \parallel R_o}{(1/g_{m2} + R_1) \parallel R_o + r_{o2}}$

In Bandgap reference, we want $\beta_n > \beta_p$ for stability purpose

when $V_x \uparrow$ $A_v(V_x - V_y) \uparrow$ so output of the opamp \uparrow . Gate voltage of $m_2 \uparrow$. PMOS current decreases \rightarrow Negative feedback.

c) $\Delta V_{BE} = V_T \ln(n)$

$V_x = V_y \Rightarrow \Delta V_{BE} = I \cdot R_1 \Rightarrow \boxed{I = \frac{V_T \ln(n)}{R_1}}$

Because M_1, M_2, M_3 are identical, current passing thru each branch is I .
so $V_{out} = I \cdot R_2$

$V_{out} = \frac{R_2}{R_1} V_T \ln(n)$

4) Single pole opamps are unconditionally stable due to only 90° phase shift

Two pole opamps are conditionally stable, phase margin may or may not satisfy enough phase margin (depends on the amplitude)

b) In order to ensure opamp is stable and do not produce any oscillation at its output

pole splitting: ω_{p1new} moved towards low freq, and ω_{p2new} moved towards high freq, so poles became far apart from each other.

c) ω_{p1}

$\frac{1}{R_{out1} \cdot C_1} = \omega_{p1}$

ω_{pout}

$R_{out} = r_{o2} \parallel r_{o1}$

$C_{total} = C_L$
 \uparrow assumed transistor capacitances are inside C_L

$\omega_{pout} = \frac{1}{(r_{o2} \parallel r_{o1}) C_L}$

d) ω_{p1new}


$\frac{1}{R_{out1} \cdot (r_1 + (1 - A_v) C_L)} = \omega_{p1new}$
 \uparrow
 $A_v = -g_{m1} (r_{o1} \parallel r_{o2})$

$\omega_{pout new}$

$C_{total} = C_L + (1 - \frac{1}{A_v}) C_L$

$R_{out} = \frac{1}{g_{m1}}$

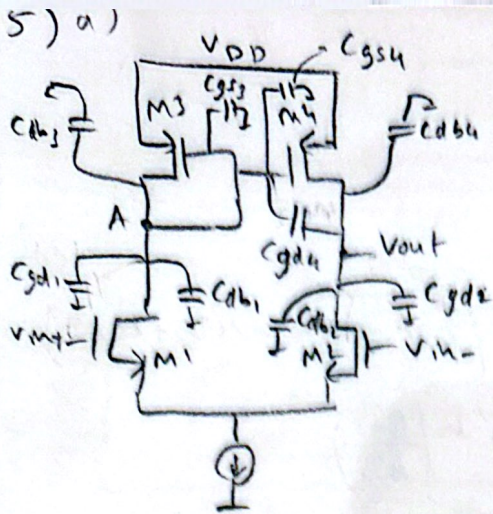$\omega_{pout new} = \frac{g_{m1}}{C_L + (1 - \frac{1}{A_v}) C_L}$



gain from A to vout

$$A_v = -g_{m4}(r_{o4} || r_{o2})$$

$$C_A = C_{gs1} + C_{db1} + C_{db3} + C_{gs2} + C_{gs4} + g_{m4}(1 - A_v)$$

$$C_{out} = C_{db2} + C_{gd2} + C_{gd4}(1 - \frac{1}{A_v}) + C_{db4}$$

$\frac{1}{g_{m3}}$

b) gain from v_{in+} to A = $-g_{m1} r_{o1} || (\frac{1}{g_{m3}} || r_{o3}) = -\frac{g_{m1}}{g_{m3}} = -1$

A to vout = $-g_{m4}(r_{o4} || r_{o2}) = -\frac{g_{m4} r_{o2}}{2}$

gain from v_{in+} to vout = $\frac{v_{out}}{v_{in+}} = \frac{g_{m4} r_{o2}}{2}$

gain from v_{in-} to vout = $-\frac{g_{m4} r_{o2}}{2} = \frac{v_{out}}{v_{in-}}$

$$\frac{v_{out}}{v_{in+}}(s) = (-1) \cdot \left(\frac{1}{1 + \frac{s}{\omega_{PA}}} \right) \cdot \left(-\frac{g_{m4} r_{o2}}{2} \right) \cdot \left(\frac{1}{1 + \frac{s}{\omega_{pout}}} \right) = \frac{g_{m4} r_{o2}}{2} \left(\frac{1}{1 + \frac{s}{\omega_{PA}}} \right) \cdot \left(\frac{1}{1 + \frac{s}{\omega_{pout}}} \right)$$

$v_{in+} \rightarrow A$ $A \rightarrow v_{out}$

$$\frac{v_{out}}{v_{in-}}(s) = -\frac{g_{m4} r_{o2}}{2} \cdot \left(\frac{1}{1 + \frac{s}{\omega_{pout}}} \right)$$

$$\frac{v_{out}}{v_{in}}(s) = \frac{g_{m4} r_{o2}}{2} \left(\frac{1}{1 + \frac{s}{\omega_{pout}}} \right) \left[\frac{1}{1 + \frac{s}{\omega_{PA}}} + 1 \right]$$

$$\omega_{PA} = \frac{1}{C_A \cdot \frac{1}{g_{m3}}} \quad \omega_{pout} = \frac{1}{C_{out} \cdot (r_{o4} || r_{o2})}$$

$$\frac{v_{out}}{v_{in}}(s) = -\frac{g_{m4} r_{o2}}{2} \cdot \frac{\left(2 + \frac{s}{\omega_{PA}} \right)}{\left(1 + \frac{s}{\omega_{PA}} \right) \cdot \left(1 + \frac{s}{\omega_{pout}} \right)}$$

For at $s = \omega_{PA} = 2 \frac{g_m}{C_A}$